
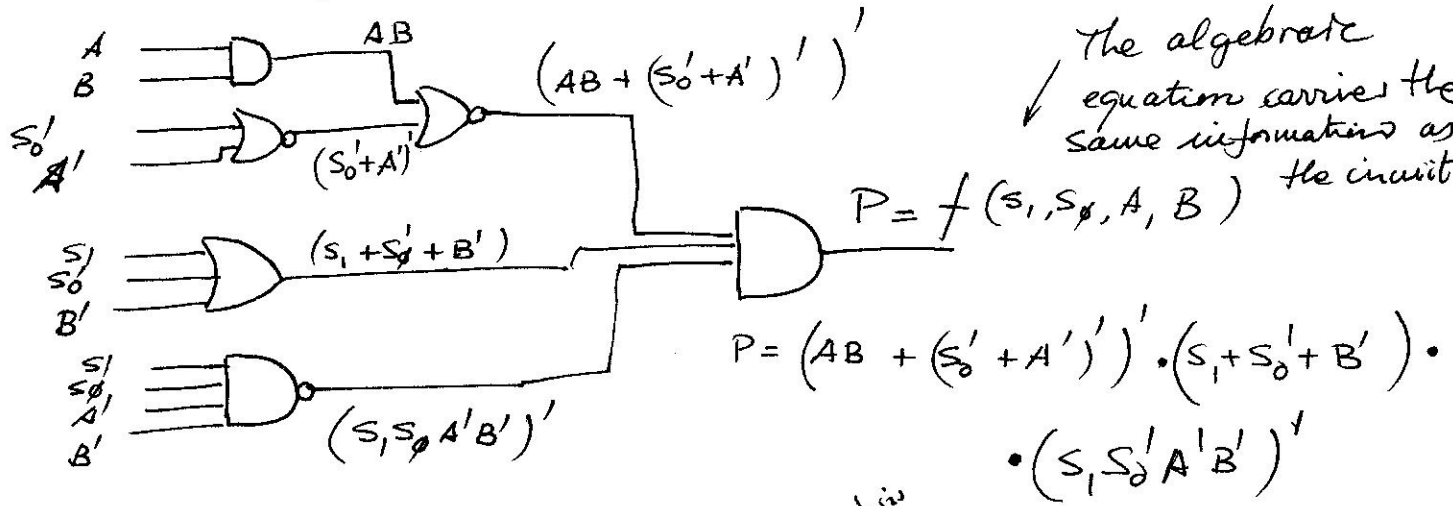


* Circuit 1A to be analysed

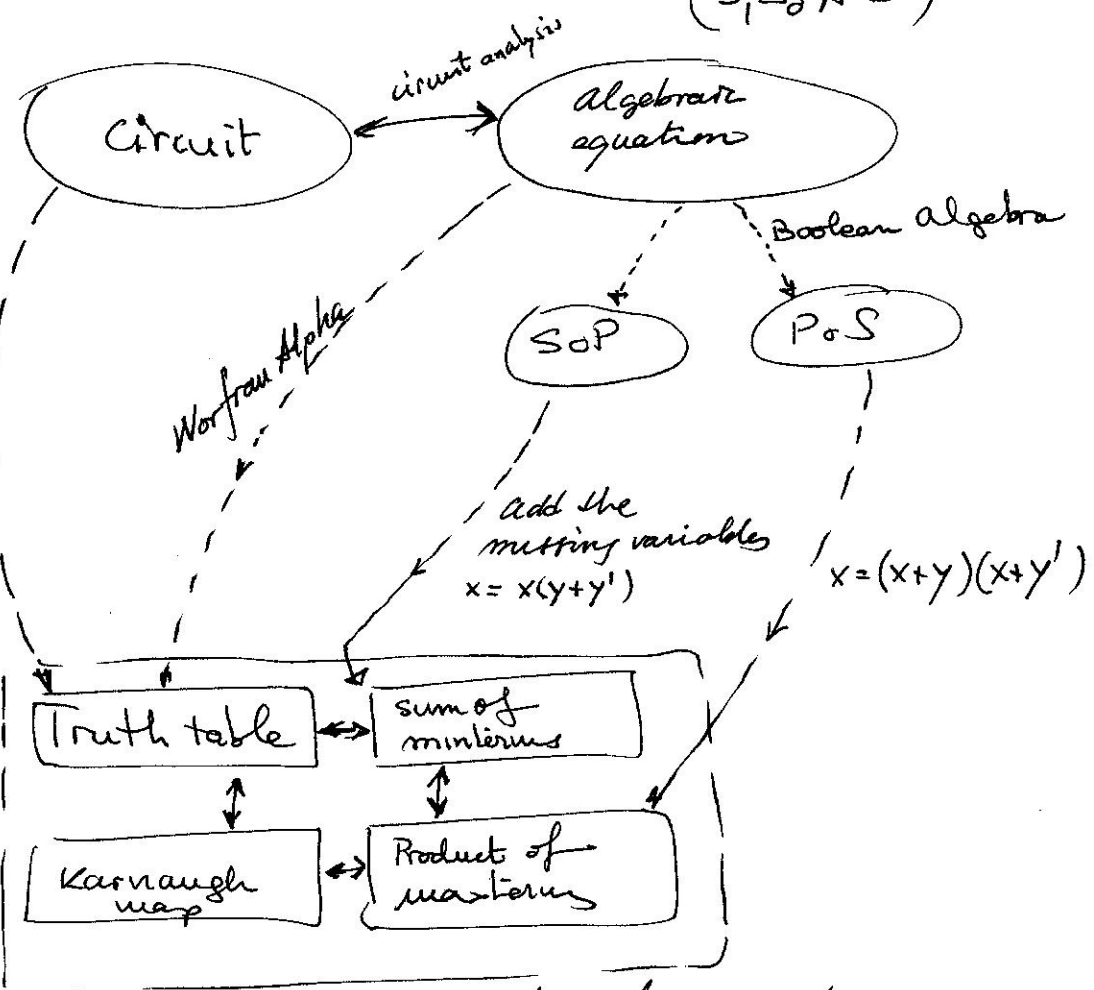

Analysis concept map as in Unit 1.3

Proteus-ICLS simulator



$$(xy)' = x' + y'$$

$$(x+y)' = x' \cdot y'$$

The set of specifications to be found by the analysis procedure

So, let's solve it analytically. Let's see how to find a SoP or a PoS. Term by term simplification:

$$(AB + (S_0' + A')')' = (AB)' \cdot (S_0' + A')'' = (A' + B')(S_0' + A')$$

So, it becomes a product of terms:

$$(S_1 S_0' A' B')' = (S_1' + S_0 + A + B)$$

PoS \rightarrow

$$P = (A'+B') \cdot (S_0'+A') \cdot (S_1+S_0'+B') \cdot (S_1'+S_0+A+B)$$

Let's add the missing variables now, in order to obtain the product of minterms

$$(A'+B') = (S_0+A'+B') (S_0'+A'+B')$$
$$(S_1+S_0+A'+B') (S_1'+S_0+A'+B') \quad (S_1+S_0'+A'+B') \cdot (S_1'+S_0'+A'+B')$$
$$M_{0011} \cdot M_{1011} \cdot M_{0011} \cdot M_{1111}$$

3 11 7 15

$$(S_0'+A') = (S_1+S_0'+A'+B) \cdot (S_1'+S_0'+A'+B')$$
$$(S_1+S_0'+A'+B) \cdot (S_1+S_0'+A'+B') \quad (S_1'+S_0'+A'+B) \cdot (S_1'+S_0'+A'+B')$$
$$M_{0110} \cdot M_{0111} \cdot M_{1110} \cdot M_{1111}$$

6 7 14 15

$$(S_1+S_0'+B') = (S_1+S_0'+A+B') \cdot (S_1+S_0'+A'+B')$$
$$M_{0101} \cdot M_{0111}$$

5 7

So, finally $P = f(S_1, S_0, A, B) = M_3 \cdot M_5 \cdot M_6 \cdot M_7 \cdot M_{11} \cdot M_{14} \cdot M_{15} \cdot M_8$

$$P = \prod_4 M(3, 5, 6, 7, 8, 11, 14, 15)$$

And: $\Rightarrow P = \sum_4 m(0, 1, 2, 4, 9, 10, 12, 13)$

$$m_4 = m_{0001} = S_1' \cdot S_0' \cdot A' \cdot B$$
$$m_9 = m_{1001} = S_1 \cdot S_0' \cdot A' \cdot B$$

Be aware!