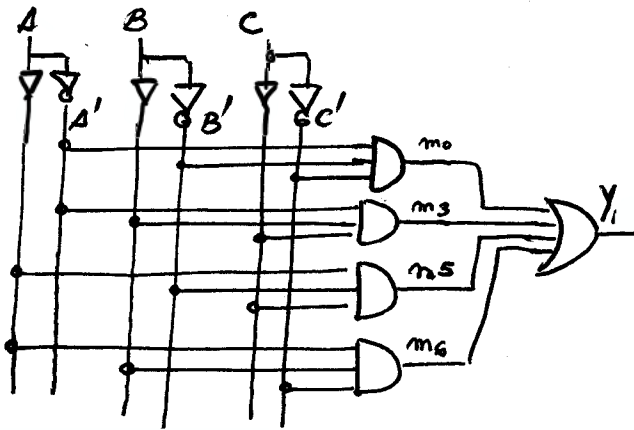


Designing logic circuits using only NAND or only NOR


This is a simple example circuit $A \rightarrow$ $B \rightarrow$ $C \rightarrow$ $\square \rightarrow Y = f(A, B, C)$

Truth table: $Y = \sum_3 m(0, 3, 5, 6) = m_0 + m_3 + m_5 + m_6 = A'B'c' + A'BC + ABC' + ABC'$

① Canonical circuit



② Circuit using only NAND

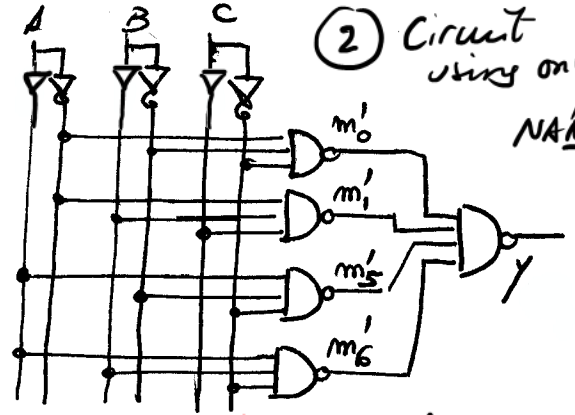


Using this transformation $\rightarrow Y = (m_0 + m_3 + m_5 + m_6)'' = (m_0' \cdot m_3' \cdot m_5' \cdot m_6')$ only \rightarrow NAND


Alternatively: ③ $Y = \prod_3 M(1, 2, 4, 7) = M_1 \cdot M_2 \cdot M_4 \cdot M_7$ (OR, AND, NOT)

and with this transformation: $Y = (M_1 \cdot M_2 \cdot M_4 \cdot M_7)'' = (M_1' + M_2' + M_4' + M_7')$ (NOR)
we have a circuit ④ $(A+B+C)'$ $(A+B+C)'$ $(A+B+C)'$ $(A'+B'+C)'$


③ Canonical circuit using maxterms

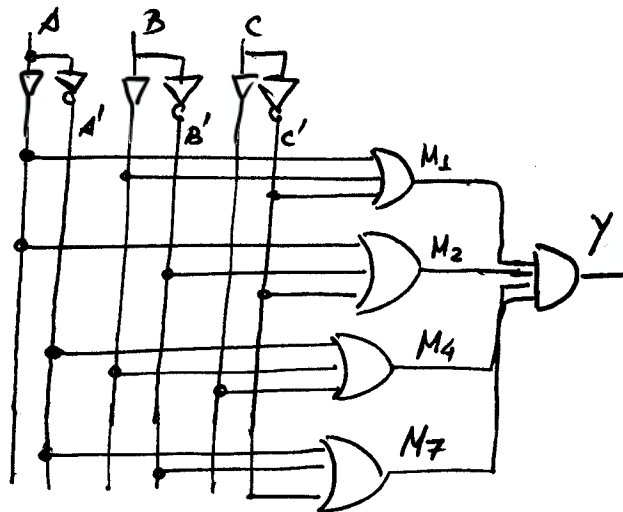

④ Using only NOR

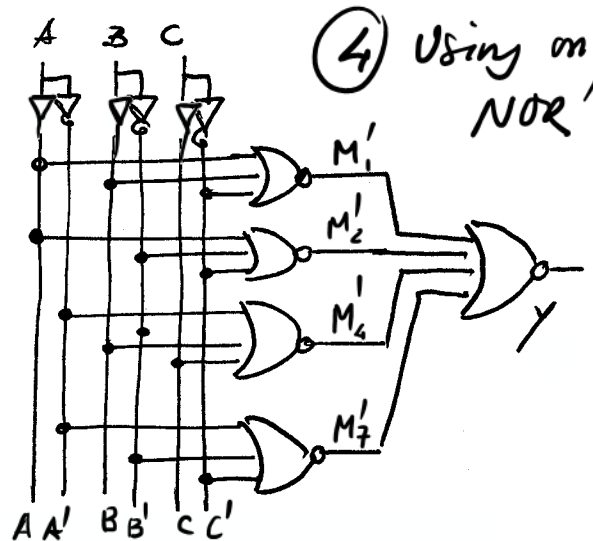

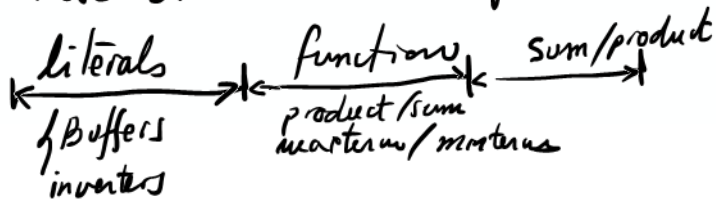These circuits have all of them 3 levels of gates



Thus, in principle, any combinational circuit can be implemented using only 3 levels of gates

Additionally to the 3 levels of gates circuits, it is also possible to use only NAND or only NOR from any expression.

For instance: from circuit (3) (canonical based on maxterms)


$$Y = \prod_3 M(1, 2, 4, 7) = M_1 \cdot M_2 \cdot M_4 \cdot M_7$$

We can implement the circuit using only NAND \rightarrow (5) adding another level of gates (a final inverter)

$$Y = (M_1'' \cdot M_2'' \cdot M_4'' \cdot M_7'')'' = ((A+B+C)'' \cdot (A+B+C)'' \cdot (A'+B+C)'' \cdot (A'+B+C)'')''$$

$$Y = ((A' \cdot B' \cdot C'')' \cdot (A' \cdot B'' \cdot C')' \cdot (A'' \cdot B' \cdot C')' \cdot (A'' \cdot B'' \cdot C'')')'$$
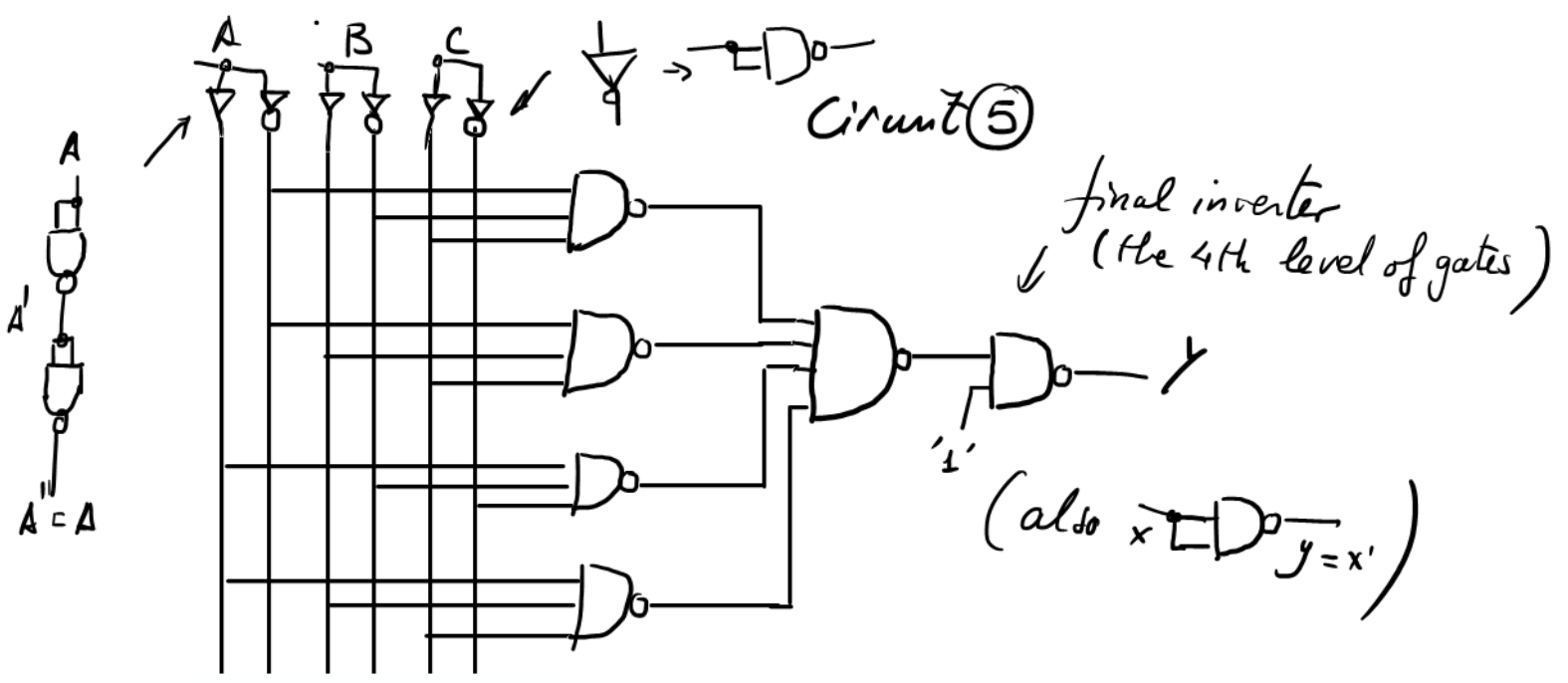
$$= ((A' \cdot B' \cdot C)' \cdot (A' \cdot B \cdot C)' \cdot (A \cdot B' \cdot C)' \cdot (A \cdot B \cdot C)')'$$



All the circuit implemented using only NAND

In the same way we can design a complete circuit which contains only NOR.

For instance, from (1)
$$Y = \sum_3 m(0,3,5,6) = (m_0'' + m_3'' + m_5'' + m_6'')$$

$$Y = \left((A \cdot B \cdot C)' + (A' \cdot B \cdot C)' + (A \cdot B' \cdot C)' + (A \cdot B \cdot C')' \right)''$$

$$Y = \left(\left((A + B + C)' + (A + B' + C)' + (A' + B + C)' + (A' + B' + C)' \right) \right)''$$

↑ NOR

↑ NOR
↑ final inversion

Circuit
⑥

