

Implementing logic functions by the method of decoders

Each decoder output is a function consisting of a single minterm of the inputs:

$$Y_i = E \cdot m_i(x) \quad 0 \leq i \leq 2^n - 1$$

In this way, it is easy to implement any logic function using a single OR


Ex: Even parity function

a b c	Y_{EP}	Y_{OP}
0 0 0	0	1
0 0 1	1	0
0 1 0	1	0
0 1 1	0	1
1 0 0	1	0
1 0 1	0	1
1 1 0	0	1
1 1 1	1	0

Odd parity function



$$Y_{EP} = f(a,b,c) = \sum_3 m(1,2,4,7)$$

$$= m_1 + m_2 + m_4 + m_7$$


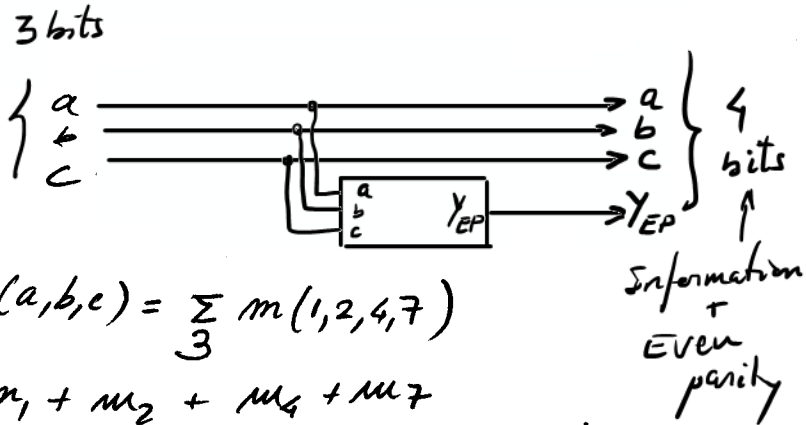


In the same way: $Y_{EP} = \left(\sum_3 m(1,2,4,7) \right)' = (m_1' \cdot m_2' \cdot m_4' \cdot m_7')$

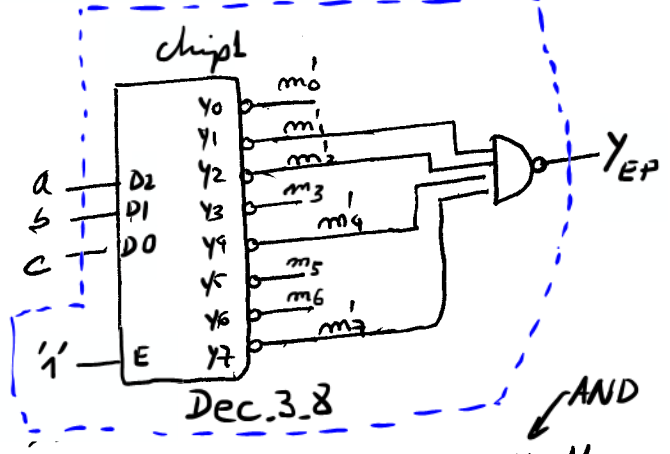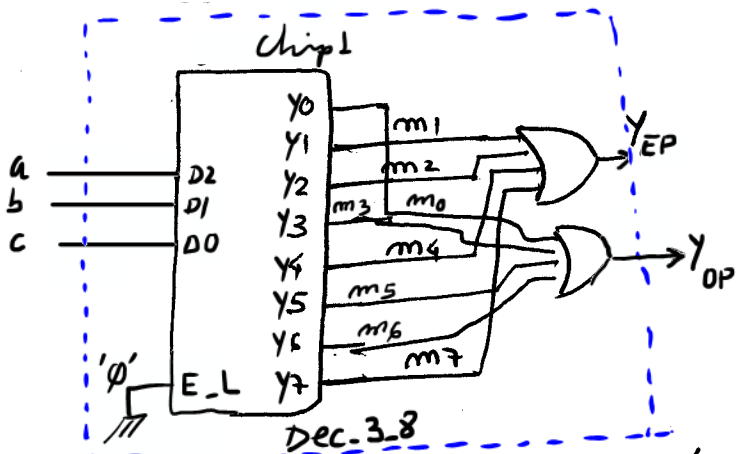Thus, if we use a decoder with active-high outputs \rightarrow OR
and if we use a decoder with active-low outputs \rightarrow NAND



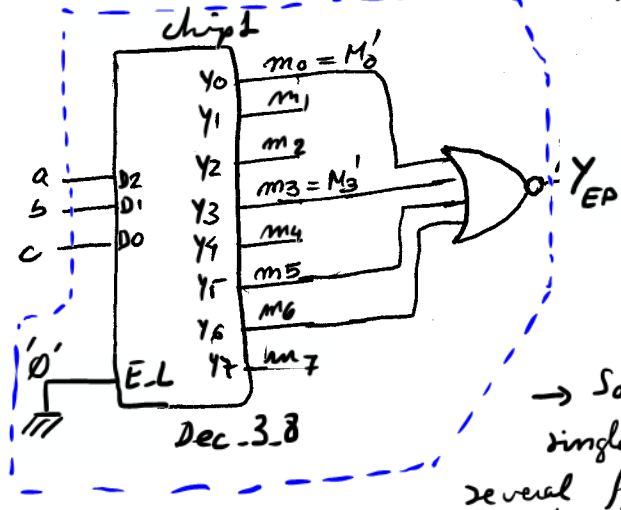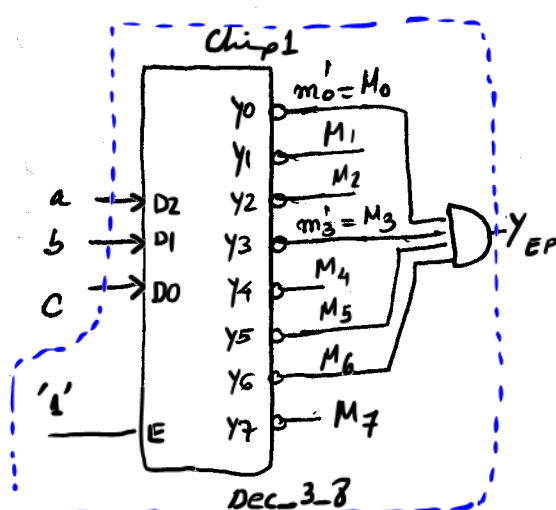If we try to implement the function based on maxterms $\rightarrow Y_{EP} = \prod_3 M(0,3,5,6) = M_0 \cdot M_3 \cdot M_5 \cdot M_6$
 $\rightarrow Y_{EP} = (M_0' + M_3' + M_5' + M_6')$



\rightarrow So, with a single decoder several functions can be implemented