



Escola d'Enginyeria de Telecomunicació
i Aeroespacial de Castelldefels



EX 3 DIGITAL CIRCUITS AND SYSTEMS

Designing a serial multiplier

1.1 Cooperative group

TEAM NUMBER: _____

DUE DATE: _____ 1st review due date: _____

STUDY TIME:

Study time (in hours)	Group work	Classroom and laboratory sessions		Sessions out of classroom	
		Individual	Student 1 Student 2 Student 3		

STATEMENT:

My signature below indicates that I have (1) made equitable contribution to EX 3 as a member of the group, (2) read and fully agree with the contents (i.e., results, conclusions, analyses, simulations) of this document, and (3) acknowledged by name anyone outside this group who assisted this learning team or any individual member in the completion of this document.

Today's date: _____

Active members

- (1) _____
 (2) _____
 (3) _____

Roles: (reporter, simulator, etc.)

Acknowledgement of individual(s) who assisted this group in completing this document:

- (1) _____
 (2) _____

1.2 Abstract

In this exercise we will perform a multiplier in VHDL. We will see each of the parts of this multiplier: a 4x4 serial multiplier, a clock divider, a timer, a binary to BCD converter of 8 bits, a quad mux4 and the BCD to 7 segment converter. We will study these parts step by step.

CONTENT

Designing a serial multiplier	1
1.1 Cooperative group	1
1.2 Abstract.....	1
1.3 Problem solution.....	3
1.3.1 <i>The structure of the top design</i>	3
1.3.2 <i>Multiplier</i>	3
1.3.2.1 <i>The 4x4 unsigned serial multiplier</i>	5
1.3.2.2 <i>The clock divider</i>	14
1.3.2.3 <i>The Timer</i>	21
1.3.2.4 <i>The Binary to BCD converter of 8 bit</i>	24
1.3.2.5 <i>The Quad_Mux4</i>	27
1.3.2.6 <i>The BCD to 7 segments</i>	27
1.3.3 <i>Total design</i>	28

1.3 Problem solution

1.3.1 The structure of the top design

For do the multiplier, we will separate the project in different blocks. These blocks will be grouped in the block that we see in Fig. 1.

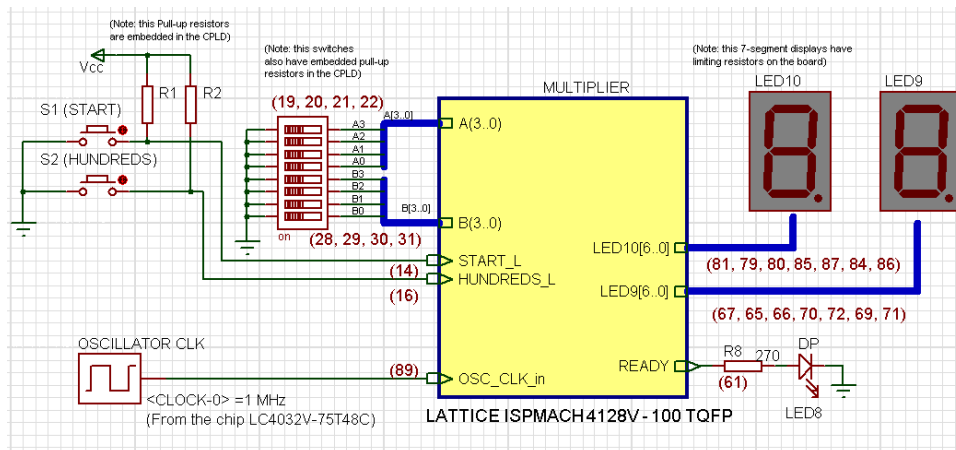


Fig. 1 Schematic of multiplier

In this schematic we can see a multiplier where LED10 show the operand A (the tens) and LED9 show the operand B (the units). Push button HUNDREDS shows the hundreds and start pulse triggers the operation. The result is displayed while READY is high (5 seconds), then the operand are shown again.

1.3.2 Multiplier

The main blocks that we will see for do the multiplier are one frequency divider, one unsigned 4 bits multiplier, one timer, one binary to BCD converter of 8 bits, two quad mux4 and two BCD to 7 segments converter. The design that we will do is in this Fig. 2.

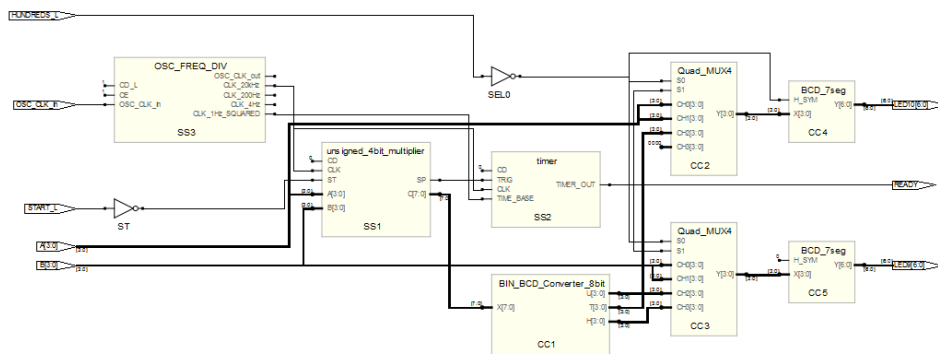


Fig. 2 Design of multiplier

For all this blocks we have a code in VHDL of the entire project in Fig. 3. This code group all the blocks that after break down one to one.

```

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;
USE IEEE.NUMERIC_STD.all;
ENTITY multiplier IS
  PORT (
    A, B : IN STD_LOGIC_VECTOR(3 DOWNTO 0); --INPUTS
    START_L : IN STD_LOGIC;
    HUNDREDS_L : IN STD_LOGIC;
    OSC_CLK_in : IN STD_LOGIC;
    LED9, LED10 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0); --OUTPUT
    READY : OUT STD_LOGIC;
  );
END multiplier;

ARCHITECTURE STRUCTURAL OF multiplier IS
  COMPONENT OSC_FREQ_DIV IS
    PORT (
      CE : IN std_logic;
      OSC_CLK_in : IN std_logic;
      CD_L : IN std_logic;
      CLK_4Hz : OUT std_logic;
      CLK_200Hz : OUT std_logic;
      CLK_20kHz : OUT std_logic;
      CLK_1Hz_SQUARED : OUT std_logic;
      OSC_CLK_out : OUT std_logic;
    );
  END COMPONENT;

  COMPONENT unsigned_4bit_multiplier IS
    PORT (
      A, B : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
      ST, CD, CLK : IN STD_LOGIC;
      C : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
      SP : OUT STD_LOGIC;
    );
  END COMPONENT;

  COMPONENT timer IS
    PORT (
      TRIG, TIME_BASE, CD, CLK : IN STD_LOGIC;
      TIMER_OUT : OUT STD_LOGIC;
    );
  END COMPONENT;

  COMPONENT Bin_BCD_Converter_8bit IS
    PORT (
      X : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
      U, T, H : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    );
  END component;

  COMPONENT Quad_MUX4 IS
    PORT (
      CH0 : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
      CH1 : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
      CH2 : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
      CH3 : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
      S0, S1 : IN STD_LOGIC;
      Y : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    );
  END component;

  COMPONENT BCD_7seg IS
    PORT (
      X : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
      H_SYM : IN STD_LOGIC;
      Y : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);
    );
  END component;

  signal Trigger, ST, CLK_4Hz, CLK_200Hz, OSC_CLK_out, CLK_20kHz, CLK_1Hz_SQUARED, SEL0, SEL1 : STD_LOGIC;
  signal C : STD_LOGIC_VECTOR(7 DOWNTO 0);
  signal U, T, H, Digit2, Digit1 : STD_LOGIC_VECTOR(3 DOWNTO 0);

BEGIN
  SS1: unsigned_4bit_multiplier
    port map(
      ST => ST,
      A => A,
      B => B,
      CD => '0',
      CLK => CLK_20kHz,
      C => C,
      SP => Trigger
    );

  SS2: timer
    port map(
      TRIG => Trigger,
      TIME_BASE => CLK_1Hz_SQUARED,
      CD => '0',
      CLK => CLK_20kHz,
      TIMER_OUT => SEL1
    );

  SS3: OSC_FREQ_DIV
    port map(
      CE => '1',
      OSC_CLK_in => OSC_CLK_in,
      CD_L => '1',
      CLK_4Hz => CLK_4Hz,
      CLK_200Hz => CLK_200Hz,
      CLK_20kHz => CLK_20kHz,
      CLK_1Hz_SQUARED => CLK_1Hz_SQUARED,
      OSC_CLK_out => OSC_CLK_out
    );

  CC1: Bin_BCD_Converter_8bit
    port map(
      X => C,
      U => U,
      T => T,
      H => H
    );

  CC2: Quad_MUX4
    port map(
      CH0 => A,
      CH1 => A,
      CH2 => T,
      CH3 => "0000",
      S0 => SEL0,
      S1 => SEL1,
      Y => Digit2
    );

  CC3: Quad_MUX4
    port map(
      CH0 => B,
      CH1 => B,
      CH2 => U,
      CH3 => H,
      S0 => SEL0,
      S1 => SEL1,
      Y => Digit1
    );

  CC4: BCD_7seg
    port map(
      X => Digit2,
      Y => LED10,
      H_SYM => SEL0
    );

  CC5: BCD_7seg
    port map(
      X => Digit1,
      Y => LED9,
      H_SYM => '0'
    );

  ST <= NOT START_L;
  READY <= SEL1;
  SEL0 <= NOT HUNDREDS_L;
END STRUCTURAL;

```

Fig. 3 Code in VHDL of multiplier

Now we study all the parts of the multiplier step by step. The first block we let's see is the 4x4 unsigned serial multiplier.

1.3.2.1 The 4x4 unsigned serial multiplier

The first block that we study has for inputs the two numbers that we want multiplier and also it has the button ST (start) for do the operations.

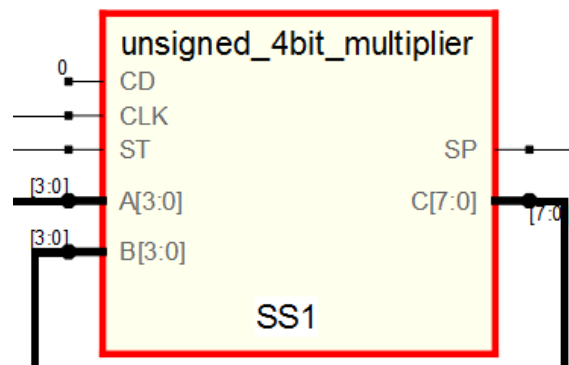


Fig. 4 Schematic of 4x4 unsigned serial multiplier

The code of this block is in Fig. 5 and we can see that this block has two others blocks within: the control unit multiplier and the datapath.

```

-----
-- Unsigned 4-bit serial multiplier
-----
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY unsigned_4bit_multiplier IS
    PORT(
        CD, CLK : IN      std_logic;
        ST      : IN      std_logic;
        A, B    : IN      std_logic_vector(3 downto 0);
        C       : OUT     std_logic_vector(7 downto 0);
        SP      : OUT     std_logic
    );
END unsigned_4bit_multiplier;

ARCHITECTURE dedicated_processor OF unsigned_4bit_multiplier IS
    COMPONENT control_unit_multiplier IS
        PORT(
            CD, CLK, ST : IN      std_logic;
            BRZ, BR0   : IN      std_logic;
            LDW, LDC   : OUT     std_logic;
            RST        : OUT     std_logic;
            SA, SB     : OUT     std_logic_vector(1 downto 0);
            SP         : OUT     std_logic
        );
    END COMPONENT;

    COMPONENT Datapath IS
        PORT(
            CD, CLK : IN      std_logic;
            SA, SB  : IN      std_logic_vector(1 downto 0);
            LDW, LDC : IN      std_logic;
            RST     : IN      std_logic;
            A, B    : IN      std_logic_vector(3 downto 0);
            C       : OUT     std_logic_vector(7 downto 0);
            BRZ, BR0 : OUT     std_logic
        );
    END COMPONENT;

    -- The internal wires to interconnect the Datapath and the Control Unit
    SIGNAL BRZ, BR0 : std_logic; -- Status from the Datapath
    SIGNAL LDW, LDC : std_logic; -- Datapath control
    SIGNAL RST      : std_logic;
    SIGNAL SA, SB   : std_logic_vector(1 downto 0);

BEGIN
    -- Instantiation of components

```

```

CU1 : control_unit_multiplier
PORT MAP (
-- from component name => to signal or port name
    CLK => CLK,
    CD  => CD,
    ST  => ST,
    SP  => SP,
    LDW => LDW,
    LDC => LDC,
    RST => RST,
    SA  => SA,
    SB  => SB,
    BRZ => BRZ,
    BR0 => BR0
);

DP1 : Datapath
PORT MAP (
-- from component name => to signal or port name
    CLK => CLK,
    CD  => CD,
    LDW => LDW,
    LDC => LDC,
    RST => RST,
    SA  => SA,
    SB  => SB,
    BRZ => BRZ,
    BR0 => BR0,
    A   => A,
    B   => B,
    C   => C
);
END dedicated_processor ;
    
```

Fig. 5 Code un VHDL of 4x4 unsigned serial multiplier

In this Fig. 6 we can see the schematic inside of the unsigned 4 bit multiplier: we have the control unit multiplier and the datapath as we have seen before.

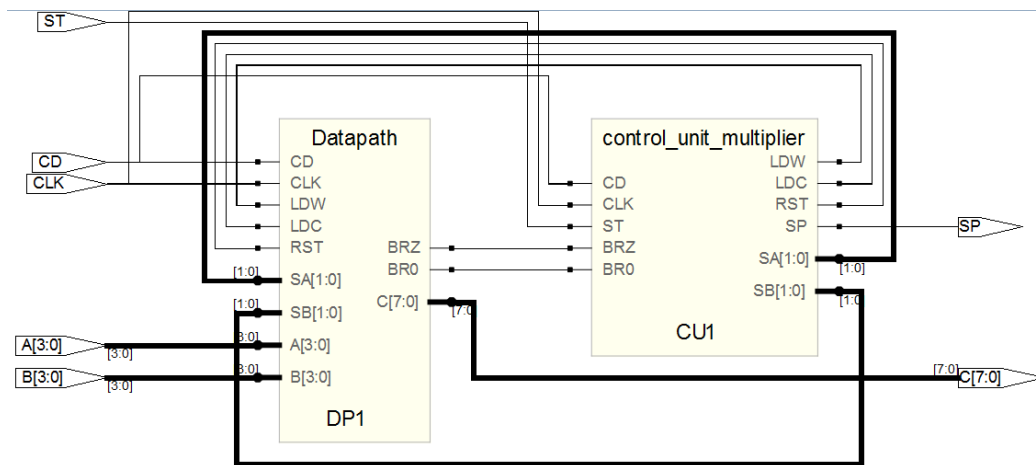


Fig. 6 Schematic inside 4x4 unsigned serial multiplier

Now we study these blocks, first the control unit multiplier and after the datapath.

1.3.2.1.1 The Control Unit Multiplier

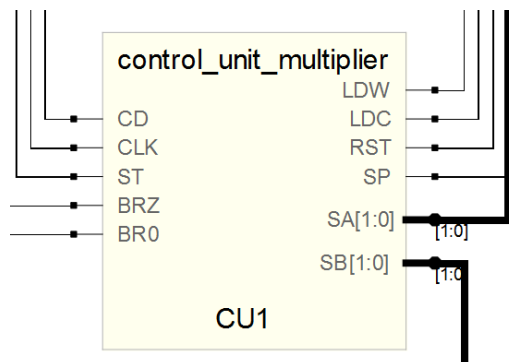


Fig. 7 Schematic of control unit multiplier

The code of the control unit multiplier is in Fig. 8

```

-----
-- Control Unit for the 4-bit unsigned multiplier
-----

LIBRARY IEEE;
USE IEEE STD_LOGIC_1164.ALL;
USE IEEE STD_LOGIC_ARITH.ALL;
USE IEEE STD_LOGIC_UNSIGNED.ALL;

ENTITY control_unit_multiplier IS
    PORT(
        CD, CLK, ST      : IN      std_logic;
        BRZ, BR0        : IN      std_logic;
        LDW, LDC        : OUT     std_logic;
        RST             : OUT     std_logic;
        SA, SB          : OUT     std_logic_vector(1 downto 0);
        SP             : OUT     std_logic
    );
END control_unit_multiplier;

ARCHITECTURE FSM_like OF control_unit_multiplier IS

    TYPE State_type IS (Idle, Load_Data, Flags, Load_Result, Add, Shift);
    -----> This is important: specifying to the synthesiser the code for the states
    ATTRIBUTE syn_enum_encoding OF State_type : STRING;
    ATTRIBUTE syn_enum_encoding OF State_type : TYPE IS "sequential";
    -- (It may be "sequential" (binary); "gray"; "one-hot", etc.
    SIGNAL present_state, future_state : State_type ;

    -- These two lines work OK, but the state machine is not recognised.
    -- and regular logic is synthesised (so it's not so good as the syn_encoding).
    -- ATTRIBUTE enum_encoding OF string;
    -- ATTRIBUTE enum_encoding OF State_type : TYPE IS "sequential";

    -- Constants for special states (the first and the last state)
    CONSTANT Reset : State_type := Idle; -- The first state. This is another name for the state Num0

BEGIN
    ----- State Register: the only clocked block.
    ----- The "memory" of the system (future events will depend on past events)

    state_register: PROCESS (CD, CLK)
    BEGIN
        IF CD = '1' THEN -- asynchronous reset of the FSM
            present_state <= Reset;
        ELSIF (CLK'EVENT and CLK = '1') THEN -- Synchronous register (D-type flip-flop)
            present_state <= future_state;
        END IF;
    END PROCESS state_register;

    ----- CC1: Combinational system for calculating next state
    CC_1: PROCESS (present_state, BR0, BRZ, ST)
    BEGIN

        CASE present_state is
            when Idle =>
                if ST='0' then
                    future_state <= Idle;
                else
                    future_state <= Load_Data ;
                end if;
            when Load_Data =>
                future_state <= Flags ;
            when Flags =>
                if BRZ='1' then
                    future_state <= Load_Result;
                elsif ( BRZ='0' and BR0='1') then
                    future_state <= Add;
                elsif ( BRZ='0' and BR0='0') then
                    future_state <= Shift;
                end if;
            when Load_Result =>
                future_state <=Idle;
            when Add =>
                future_state <=Shift;
            when Shift =>
                future_state <=Flags;
        end case;
    END PROCESS CC_1;

    ----- CS_2: combinational system for calculating extra outputs
    ----- and outputting the present state (the actual count)
    CC_2: PROCESS (present_state)
    BEGIN
        CASE present_state is
            when Idle =>
                LDW <='0';
                LDC <='0';
                RST <='0';
                SA <="00";
                SB <="00";
                SP <='0';
            when Load_Data =>
                LDW <='0';
                LDC <='0';
                RST <='1';
                SA <="11";
                SB <="11";
                SP <='0';
            when Flags =>
                LDW <='0';
                LDC <='0';
                RST <='0';
                SA <="00";
                SB <="00";
                SP <='0';
            when Load_Result =>
                LDW <='0';
                LDC <='1';
                RST <='0';
                SA <="00";
                SB <="00";
                SP <='1';
            when Add =>
                LDW <='0';
                LDC <='0';
                RST <='0';
                SA <="00";
                SB <="00";
                SP <='0';
        end case;
    END PROCESS CC_2;
END ARCHITECTURE FSM_like;

```

```

LDW <='1';
LDC <='0';
RST <='0';
SA <='00';
SB <='00';
SP <='0';

when Shift =>
LDW <='0';
LDC <='0';
RST <='0';
SA <='10';
SB <='01';
SP <='0';
end case;

END PROCESS CC_2;

-- Place other logic if necessary

END FSM_like;

```

Fig. 8 Code in VHDL of control unit multiplier

1.3.2.1.2 The Datapath

The second block of the 4x4 unsigned serial multiplier is the datapath that we have in Fig. 9.

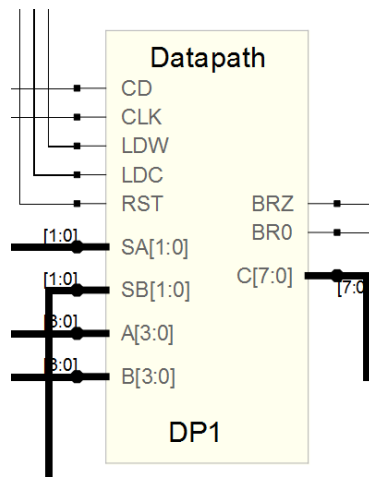


Fig. 9 Schematic of datapath

Below, for understand that we do, we have in Fig. 10 the flow diagram (while designing the datapath) for do the corresponding code.

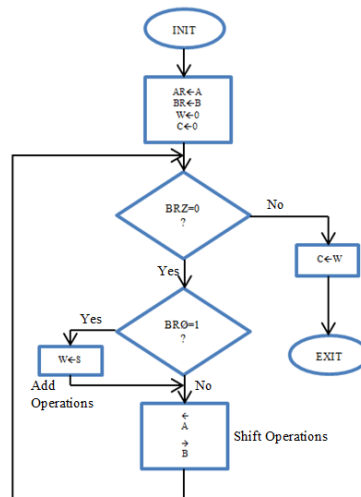


Fig. 10 Diagram of datapath

With this diagram we can do the code in VHDL that we have in Fig. 11.

```

-- 4-bit unsigned multiplier datapath
-- Structural and hierarchical design

LIBRARY ieee;
USE IEEE.Std_Logic_1164.all;

ENTITY Datapath IS
  PORT(
    CD,CLK : IN std_logic;
    SA, SB : IN std_logic_vector(1 downto 0);
    LDW, LDC : IN std_logic;
    RST : IN std_logic;
    A, B : IN std_logic_vector(3 downto 0);
    C : OUT std_logic_vector(7 downto 0);
    BRZ, BR0 : OUT std_logic
  );
END Datapath;

ARCHITECTURE Structural OF Datapath IS
  -- Components

  COMPONENT Shift_Data_Reg_4bits IS
    PORT(
      CD,CLK : IN std_logic;
      X : IN std_logic_vector(3 downto 0);
      Y : OUT std_logic_vector(3 downto 0);
      S : IN std_logic_vector(1 downto 0);
      RSI,LSI : IN std_logic
    );
  END COMPONENT;

  COMPONENT Shift_Data_Reg_8bits IS
    PORT(
      CD,CLK : IN std_logic;
      X : IN std_logic_vector(7 downto 0);
      Y : OUT std_logic_vector(7 downto 0);
      S : IN std_logic_vector(1 downto 0);
      RSI,LSI : IN std_logic
    );
  END COMPONENT;

  COMPONENT Data_Reg_8bit IS
    Port (
      CLK : IN STD_LOGIC;
      CD : IN STD_LOGIC;
      RST : IN STD_LOGIC;
      LD : IN STD_LOGIC;
      Y : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
      X : IN STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
  END COMPONENT;

  COMPONENT Adder_8bit IS
    PORT (
      A,B : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
      Ci : IN STD_LOGIC;
      S : OUT STD_LOGIC_VECTOR (7 DOWNTO 0);
      Co : OUT STD_LOGIC
    );
  END COMPONENT;

  -- Internal wires
  SIGNAL S, W, AR : STD_LOGIC_VECTOR(7 downto 0);
  SIGNAL BR : STD_LOGIC_VECTOR(3 downto 0);
  SIGNAL Co : STD_LOGIC;

BEGIN
  -- Instantiation of components
  RegW : Data_Reg_8bit
  PORT MAP (
    -- from component name => to signal or port name
    CLK => CLK,
    CD => CD,
    RST => RST,
    LD => LDW,
    Y => W,
    X => S
  );

  RegC : Data_Reg_8bit
  PORT MAP (
    -- from component name => to signal or port name
    CLK => CLK,
    CD => CD,
    RST => RST,
    LD => LDC,
    Y => C,
    X => W
  );

  RegA : Shift_Data_Reg_8bits
  PORT MAP (
    -- from component name => to signal or port name
    CLK => CLK,
    CD => CD,
    Y => AR,
    X (3 downto 0) => A,
    X (7 downto 4) => "0000",
    S => SA,
    RSI => '0',
    LSI => '0'
  );

  RegB : Shift_Data_Reg_4bits
  PORT MAP (
    -- from component name => to signal or port name
    CLK => CLK,
    CD => CD,
    Y => BR,
    X => B,
    S => SB,
    RSI => '0',
    LSI => '0'
  );

  Adder8 : Adder_8bit
  PORT MAP (
    -- from component name => to signal or port name
    A => AR,
    B => W,
    S => S,
    Ci => '0',
    Co => Co
  );

  -- Extra logic in the circuit
  BRZ <= NOT( BR(0) OR BR(1) OR BR(2) OR BR(3));
  BR0 <= BR(0);

END Structural;

```

Fig. 11 Code in VHDL of datapath

Inside of this block we have the adder, the datareg 8 bit, the shift data register of 4 bit and the shift data register of 8 bit. We can see this in Fig. 12 and below we study this blocks step by step.

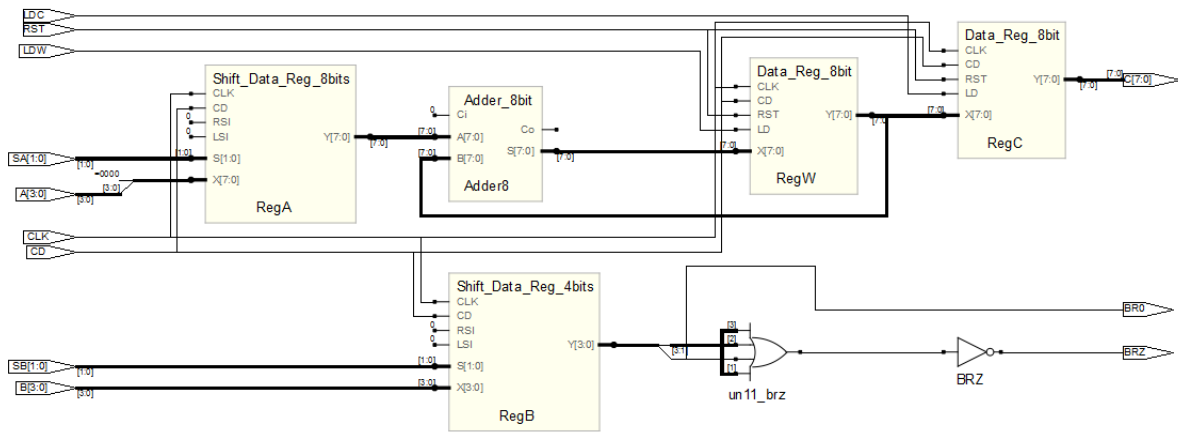


Fig. 12 Schematic inside the datapath

1.3.2.1.2.1 The Adder

We have study an adder previously and we know that an adder of 8 bits it compounded of four adder of two bits or, in this case, we have eight adders of 1 bit. Firt we see the 8 bit adder that we can see in Fig. 13.

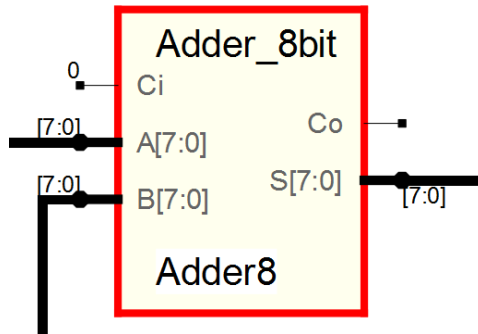


Fig. 13 Schematic of adder

The code of the 8 bit adder is in Fig. 14 and we can see the 8 adder that we need for do this part of the multiplier.

```

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;

ENTITY Adder_8bit IS
    PORT ( A,B      : IN  STD_LOGIC_VECTOR(7 DOWNTO 0);
          Ci      : IN  STD_LOGIC;
          S       : OUT STD_LOGIC_VECTOR (7 DOWNTO 0);
          Co      : OUT STD_LOGIC
    );
END Adder_8bit;

ARCHITECTURE estructura_en_cascada OF Adder_8bit IS
    COMPONENT One_bit_adder IS
        PORT ( Ai,Bi,Ci      : IN STD_LOGIC;
              So,Co        : OUT STD_LOGIC
        );
    END COMPONENT;

    SIGNAL C1, C2, C3, C4,C5, C6, C7, C8 : STD_LOGIC; -- The wires to connect 1-bit modules together
    SIGNAL Y : STD_LOGIC_VECTOR (7 DOWNTO 0);

BEGIN
    adder_0 : One_bit_adder
        PORT MAP (
            Ai      => A(0),
            Bi      => B(0),
            Ci      => Ci,
            So      => Y(0),
            Co      => C1
        );

    adder_1 : One_bit_adder
        PORT MAP (
            Ai      => A(1),
            Bi      => B(1),
            Ci      => C1,
            So      => Y(1),
            Co      => C2
        );

    adder_2 : One_bit_adder
        PORT MAP (
            Ai      => A(2),
            Bi      => B(2),
            Ci      => C2,
            So      => Y(2),
            Co      => C3
        );

    adder_3 : One_bit_adder
        PORT MAP (
            Ai      => A(3),
            Bi      => B(3),
            Ci      => C3,
            So      => Y(3),
            Co      => C4
        );

    adder_4 : One_bit_adder
        PORT MAP (
            Ai      => A(4),
            Bi      => B(4),
            Ci      => C4,
            So      => Y(4),
            Co      => C5
        );

    adder_5 : One_bit_adder
        PORT MAP (
            Ai      => A(5),
            Bi      => B(5),
            Ci      => C5,
            So      => Y(5),
            Co      => C6
        );

    adder_6 : One_bit_adder
        PORT MAP (
            Ai      => A(6),
            Bi      => B(6),
            Ci      => C6,
            So      => Y(6),
            Co      => C7
        );

    adder_7 : One_bit_adder
        PORT MAP (
            Ai      => A(7),
            Bi      => B(7),
            Ci      => C7,
            So      => Y(7),
            Co      => C8
        );

    S <= Y;
    Co <= C8;
END estructura_en_cascada;

```

Fig. 14 Code in VHDL of adder

Inside of this adder we have the one bit adders that we speak previously.

1.3.2.1.2.1.1 One bit adder

 


Fig. 15 Schematic of one bit adders

The code that we see in Fig. 16 of the one bit adder is exactly the code that we see in the previous chapter.

```

-----
-- A One-bit adder using logic equations (structural)
-----

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;

ENTITY One_bit_adder IS
    PORT (
        Ai, Bi, Ci : IN STD_LOGIC;
        So, Co      : OUT STD_LOGIC
    );
END One_bit_adder;

ARCHITECTURE logic_equations OF One_bit_adder IS

BEGIN
    So <= Ai XOR Bi XOR Ci;
    Co <= (Ai AND Bi) OR (Ci AND (Ai OR Bi));
END logic_equations ;

```

Fig. 16 Code in VHDL of one bit adder

1.3.2.1.2.2 The DataReg 8 bit

The next block we are study is the data register of 8 bits that we see in Fig. 17.

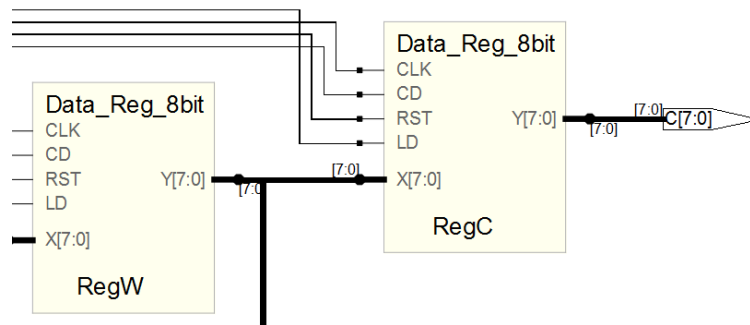


Fig. 17 Schematic of datareg 8 bit

The code of the datareg 8 bit is in Fig. 18 and we can see that if clear direct is '1' we have a all zeros, if it is '0' we pass to the future state, if RST is '1' we have a reset, and if LD is '1' we load a number X in future state.

```

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;
USE IEEE.STD_LOGIC_ARITH.all;
USE IEEE.STD_LOGIC_UNSIGNED.all;

ENTITY Data_Reg_8bit IS
    Port (
        CLK : IN STD_LOGIC;
        CD  : IN STD_LOGIC;
        RST : IN STD_LOGIC;
        LD  : IN STD_LOGIC;
        Y   : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        X   : IN STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
END Data_Reg_8bit;

ARCHITECTURE FSM_like OF Data_Reg_8bit IS
    CONSTANT Reset : STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000000";
    SIGNAL present_state, future_state: STD_LOGIC_VECTOR(7 DOWNTO 0);
    BEGIN
        State_Register: PROCESS (CD, CLK)
            BEGIN
                IF CD = '1' THEN
                    present_state <= Reset;
                ELSIF (CLK'EVENT and CLK = '1') THEN
                    present_state <= future_state;
                END IF;
            END PROCESS State_Register;

        CC1: PROCESS (present_state, X, RST, LD)
            BEGIN
                IF RST = '1' THEN
                    future_state <= Reset;
                ELSIF LD = '1' THEN
                    future_state <= X;
                ELSE
                    future_state <= present_state;
                END IF;
            END PROCESS CC1;

        Y <= present_state;
    END FSM_like;

```

Fig. 18 Code in VHDL of datareg 8 bit

1.3.2.1.2.3 The Shift DataReg 4 bit

The shift datareg that we have in Fig. 19 is very similar to datareg but now the numbers are moved to left or right.

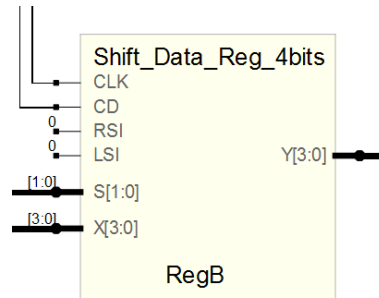


Fig. 19 Schematic of Shift DataReg 4 bit

This is the true table of this block, depending on the value of S1 and S0 in future state we have or present state, or a number loaded, or the number moved to right or left.

S1	S0	Y ⁺
0	0	Y
0	1	→
1	0	←
1	1	Load data

Fig. 20 True table of Shift DataReg 4 bit

In Fig. 21 we have the code of the Shift DataReg 4 bit and here we can see how to do this true table in code VHDL.

```

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY Shift_Data_Reg_4bits IS
    Port (
        CLK      : IN  STD_LOGIC;
        CD       : IN  STD_LOGIC;
        S        : IN  STD_LOGIC_VECTOR(1 DOWNTO 0);
        RSI      : IN  STD_LOGIC;
        LSI      : IN  STD_LOGIC;
        Y        : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
        X        : IN  STD_LOGIC_VECTOR(3 DOWNTO 0)
    );
END Shift_Data_Reg_4bits;
ARCHITECTURE FSM_like OF Shift_Data_Reg_4bits IS
    CONSTANT Reset : STD_LOGIC_VECTOR(3 DOWNTO 0) := "0000";
    SIGNAL present_state, future_state : STD_LOGIC_VECTOR(3 DOWNTO 0);
    BEGIN
    State_Register: PROCESS (CD, CLK)
        BEGIN
            IF CD = '1' THEN
                present_state <= Reset; -- reset counter ( an asynchronous reset which we call "Clear Direct"
            ELSIF (CLK'EVENT and CLK = '1') THEN
                present_state <= future_state; -- Synchronous register (D-type flip-flop)
            END IF;
        END PROCESS State_Register;

    CC1: PROCESS (present_state, X, S, RSI, LSI)
        BEGIN
            IF S = "11" THEN
                future_state <= X;
            ELSIF S = "01" THEN
                future_state(0) <= present_state(1);
                future_state(1) <= present_state(2);
                future_state(2) <= present_state(3);
                future_state(3) <= RSI;
            ELSIF S = "10" THEN
                future_state(3) <= present_state(2);
                future_state(2) <= present_state(1);
                future_state(1) <= present_state(0);
                future_state(0) <= LSI;
            ELSE
                future_state <= present_state;
            END IF;
        END PROCESS CC1;
    Y <= present_state;
END FSM_like;

```

Fig. 21 Code in VHDL of Shift DataReg 4 bit

1.3.2.1.2.4 The Shift DataReg 8 bit

This block is the same that the Sift DataReg 4 bit, but with 8 bits.

 


Fig. 22 Schematic of Shift DataReg 8 bit

The code of the Shift DataReg 8 bit is in Fig. 23. Is exactly to the previous code but now we have more bits.

```

LIBRARY ieee;
USE IEEE.Std_Logic_1164.all;
USE IEEE.Std_Logic_Arith.all;
USE IEEE.Std_Logic_Unsigned.all;
ENTITY Shift_Data_Reg_8bits IS
    Port (
        CLK      : IN  STD_LOGIC;
        CD       : IN  STD_LOGIC;
        S        : IN  STD_LOGIC_VECTOR(1 DOWNTO 0);
        RSI      : IN  STD_LOGIC;
        LSI      : IN  STD_LOGIC;
        Y        : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        X        : IN  STD_LOGIC_VECTOR(7 DOWNTO 0);
    );
END Shift_Data_Reg_8bits;
ARCHITECTURE FSM_like OF Shift_Data_Reg_8bits IS
    CONSTANT Reset : STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000000";
    SIGNAL present_state, future_state: STD_LOGIC_VECTOR(7 DOWNTO 0);
BEGIN
    State_Register: PROCESS (CD, CLK)
    BEGIN
        IF CD = '1' THEN
            present_state <= Reset; -- reset counter ( an asynchronous reset which we call "Clear Direct"
        ELSIF (CLK'EVENT and CLK = '1') THEN
            present_state <= future_state; -- Synchronous register (D-type flip-flop)
        END IF;
    END PROCESS State_Register;
    CCl: PROCESS (present_state, X, S, RSI, LSI)
    BEGIN
        IF S = "11" THEN
            future_state <= X;
        ELSIF S="01" THEN
            future_state(0) <= present_state(1);
            future_state(1) <= present_state(2);
            future_state(2) <= present_state(3);
            future_state(3) <= present_state(4);
            future_state(4) <= present_state(5);
            future_state(5) <= present_state(6);
            future_state(6) <= present_state(7);
            future_state(7) <= RSI;
        ELSIF S="10" THEN
            future_state(7) <= present_state(6);
            future_state(6) <= present_state(5);
            future_state(5) <= present_state(4);
            future_state(4) <= present_state(3);
            future_state(3) <= present_state(2);
            future_state(2) <= present_state(1);
            future_state(1) <= present_state(0);
            future_state(0) <= LSI;
        ELSE
            future_state <= present_state;
        END IF;
    END PROCESS CCl;
    Y <= present_state;
END FSM_like;

```

Fig. 23 Code in VHDL of Shift DataReg 8 bit

1.3.2.2 The clock divider

The next block is the clock divider that we can see in Fig. 24.

 


Fig. 24 Schematic of clock divider

We have already study this block in another exercise and we know that this block have 5 blocks inside. In Fig. 25 we can see the code of the clock divider where we can see the others blocks.

```

LIBRARY IEEE;
USE IEEE.Std_Logic_1164.ALL;
USE IEEE.Std_Logic_Arith.ALL;
USE IEEE.Std_Logic_Unsigned.ALL;

ENTITY OSC_FREQ_DIV IS
    PORT(
        CD_L,CE : IN std_logic;
        OSC_CLK_in : IN std_logic;
        OSC_CLK_out : OUT std_logic;
        CLK_20kHz : OUT std_logic;
        CLK_200Hz : OUT std_logic;
        CLK_4Hz : OUT std_logic;
        CLK_1Hz_SQUARED : OUT std_logic;
        DISPLAYS : OUT std_logic_vector(14 downto 0);
    );
-- This DISPLAYS vector is an extra output only to blank unused LED's and segments
-- In this example, only the decimal point in LED9 is used
END OSC_FREQ_DIV;

ARCHITECTURE schematic OF OSC_FREQ_DIV IS
-- Components

    COMPONENT Freq_Div_50 IS
        PORT(
            CD,CLK,CE : IN std_logic;
            TC50 : OUT std_logic
        );
    END COMPONENT;

    COMPONENT Freq_Div_100 IS
        PORT(
            CD,CLK,CE : IN std_logic;
            TC100 : OUT std_logic
        );
    END COMPONENT;

    COMPONENT Freq_Div_2 IS
        PORT(
            CD,CLK,CE : IN std_logic;
            TC2 : OUT std_logic
        );
    END COMPONENT;

    COMPONENT T_Flip_Flop IS
        PORT(
            CLK : IN std_logic;
            CD : IN std_logic;
            T : IN std_logic;
            Q : OUT std_logic
        );
    END COMPONENT;

-- Signals for connecting components together (just the internal wires)
    SIGNAL CD, OSC_CLK : std_logic;
    SIGNAL CE2, CE3, CE4, CE5 : std_logic;

BEGIN
-- Instantiation of components
    SS1 : Freq_Div_50
        PORT MAP (
-- from component name => to signal or port name
            CLK => OSC_CLK,
            CD => CD,
            CE => CE,
            TC50 => CE2
        );

    SS2 : Freq_Div_100
        PORT MAP (
-- from component name => to signal or port name
            CLK => OSC_CLK,
            CD => CD,
            CE => CE2,
            TC100 => CE3
        );

    SS3 : Freq_Div_50
        PORT MAP (
-- from component name => to signal or port name
            CLK => OSC_CLK,
            CD => CD,
            CE => CE3,
            TC50 => CE4
        );

    SS4 : Freq_Div_2
        PORT MAP (
-- from component name => to signal or port name
            CLK => OSC_CLK,
            CD => CD,
            CE => CE4,
            TC2 => CE5
        );

    SS5 : T_Flip_Flop
        PORT MAP (
-- from component name => to signal or port name
            CLK => OSC_CLK,
            CD => CD,
            T => CE5,
            Q => CLK_1Hz_SQUARED
        );

-- connections and logic between components
-- The circuit's signals that have to be connected to input ports
    OSC_CLK <= OSC_CLK_in;
    CD <= NOT(CD_L);

-- The output ports that have to be connected to signals
    OSC_CLK_out <= OSC_CLK;
    CLK_20kHz <= CE2;
    CLK_200Hz <= CE3;
    CLK_4Hz <= CE4;

-- Displays OFF when high. In this fashion, only the SQUARED LED will be ON/OFF
-- DISPLAYS <= "1111111111111111";

END schematic ;

```

Fig. 25 Code in VHDL of the clock divider

Inside the clock divider we have two frequency dividers by 50, a frequency divider by 100, a frequency divider by 2 and one T_Flip_Flop that we study now step by step that we can see in Fig. 26.

 


Fig. 26 Schematic inside the clock divider

1.3.2.2.1 The frequency divider by 50

In this part we perform a frequency divider by 50.

 


Fig. 27 Schematic of frequency divider by 50

At first we will see the ideal case, as in Active-HDL we didn't observe any delay. In Fig. 28 we have the code in VHDL of the ideal case.

```

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY Freq_Div_50 IS
    Port (
        CLK      : IN  STD_LOGIC;
        CD       : IN  STD_LOGIC;
        CE       : IN  STD_LOGIC;
        -- Q      : OUT STD_LOGIC_VECTOR(23 DOWNTO 0);
        TC50     : OUT STD_LOGIC
    );
END Freq_Div_50;

-- Internal description in FSM style
ARCHITECTURE FSM_like OF Freq_Div_50 IS
    -- This is the real and necessary Max_Count:
    -- CONSTANT Max_Count : STD_LOGIC_VECTOR(23 DOWNTO 0) := "110000000001000111101011"; -- terminal_count after 10 states 12587500
    -- This is the the Max_Count modified to speed simulations:
    -- So you must comment this line and activate the above one if you plan to use the real UP2 board
    CONSTANT Max_Count : STD_LOGIC_VECTOR(5 DOWNTO 0) := "110001";

    CONSTANT Reset      : STD_LOGIC_VECTOR(5 DOWNTO 0) := "000000"; -- 1100 0000 0001 0001 1110 1100 --1100 0000 0001 0001 1110 1011

    -- Internal wires
    SIGNAL present_state, future_state: STD_LOGIC_VECTOR(5 downto 0) := Reset;

    BEGIN
    state_register: PROCESS (CD, CLK)
    BEGIN
        IF CD = '1' THEN
            present_state <= Reset; -- reset counter
        ELSIF (CLK'EVENT and CLK = '1') THEN -- Synchronous register (D-type flip-flop)
            present_state <= future_state;
        END IF;
    END PROCESS state_register;

    ----- ESS state_registercombinational system for calculating next state
    CS_1: PROCESS (present_state, CE)
    BEGIN
        IF CE = '1' THEN
            IF (present_state < Max_Count) THEN
                future_state <= present_state + 1;
            ELSE
                future_state <= Reset;
            END IF;
        ELSE
            future_state <= present_state; -- count disable
        END IF;
    END PROCESS CS_1;

    ----- CS_2: combinational system for calculating extra outputs
    ----- and outputting the present state (the actual count)
    TC50 <= '1' WHEN (present_state = Max_Count) AND CE = '1' ELSE '0'; -- terminal count
    -- Q <= present_state; In this application, there is no need to output the count value Q

END FSM_like;

```

Fig. 28 Code in VHDL of frequency divider by 50

As we shall see in Fig. 29, we speak of an ideal system. If we do a zoom we can see no delay from CLK to TC10.

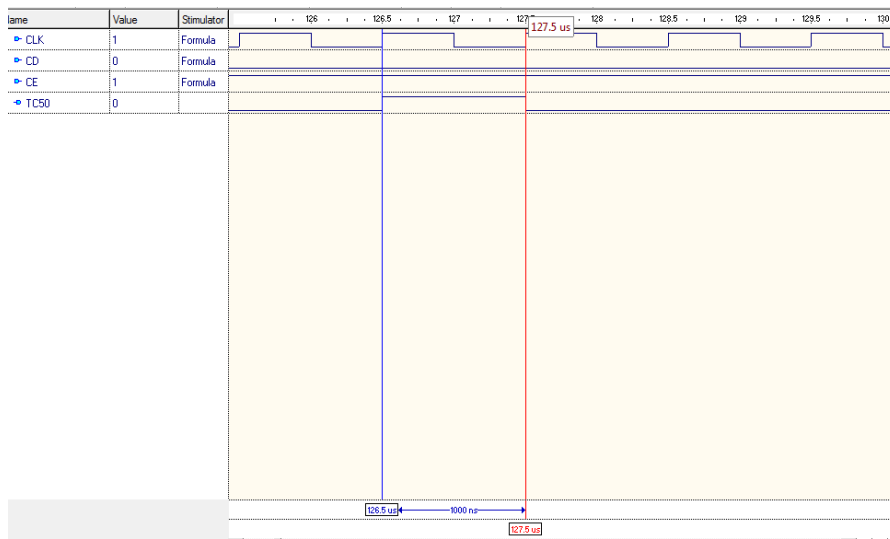


Fig. 29 Simulation ideal frequency divider by 50

And now, in Fig. 30, we let's see the case in which we observe this delay. For this we need create the .vho and the .sdf files. Once created these files we see the next simulation.

 


Fig. 30 Simulation real frequency divider by 50

Now we can see clearly that a delay exist from the clock give a pulse until the output reply to this pulse. In this case we have a delay of 8000 ps.

1.3.2.2.2 The frequency divider by 100

Now we will perform a frequency divider by 100 that we see in Fig. 31.

 


Fig. 31 Schematic of frequency divider by 100

We'll see the same that the previous case but with TC100 pulses every 100 clock's. In we see the VHDL code of the divisor.

```

LIBRARY ieee;
USE IEEE STD_LOGIC_1164.all;
USE IEEE STD_LOGIC_ARITH.all;
USE IEEE STD_LOGIC_UNSIGNED.all;

ENTITY Freq_Div_100 IS
  Port (
    CLK      : IN   STD_LOGIC;
    CD       : IN   STD_LOGIC;
    CE       : IN   STD_LOGIC;
    Q        : OUT  STD_LOGIC_VECTOR(23 DOWNTO 0);
    TC100    : OUT  STD_LOGIC
  );
END Freq_Div_100;

-- Internal description in FSM style
ARCHITECTURE FSM_like OF Freq_Div_100 IS
  -- This is the real and necessary Max_Count;
  -- CONSTANT Max_Count : STD_LOGIC_VECTOR(23 DOWNTO 0) := "110000000001000111101011"; -- terminal_count after 10 states 12587500
  -- This the the Max_Count modified to speed simulations.
  -- So you must comment this line and activate the above one if you plan to use the real UP2 board
  CONSTANT Max_Count : STD_LOGIC_VECTOR(6 DOWNTO 0) := "1100100";

  CONSTANT Reset      : STD_LOGIC_VECTOR(6 DOWNTO 0) := "0000000"; -- 1100 0000 0001 0001 1110 1100 --1100 0000 0001 0001 1110 1011
  -- Internal wires
  SIGNAL present_state,future_state: STD_LOGIC_VECTOR(6 downto 0) := Reset;

BEGIN
  ----- the only clocked block : the state register
  state_register: PROCESS (CD, CLK)
  BEGIN
    IF CD = '1' THEN -- reset counter
      present_state <= Reset;
    ELSIF (CLK EVENT and CLK = '1') THEN -- Synchronous register (D-type flip-flop)
      present_state <= future_state;
    END IF;
  END PROCESS state_register;

  ----- BSS state_registercombinational system for calculating next state
  CS_1: PROCESS (present_state, CE)
  BEGIN
    IF CE = '1' THEN
      IF (present_state < Max_Count) THEN
        future_state <= present_state + 1;
      ELSE
        future_state <= Reset;
      END IF;
    ELSE
      future_state <= present_state; -- count disable
    END IF;
  END PROCESS CS_1;

  ----- CS_2: combinational system for calculating extra outputs
  ----- and outputting the present state (the actual count)
  TC100 <= '1' WHEN ((present_state = Max_Count)AND CE = '1') ELSE '0'; --terminal count
  -- Q <= present_state; In this application, there is no need to output the count value Q

END FSM_like;

```

Fig. 32 Code in VHDL of frequency divider by 100

In the simulation we have again two cases, first is the ideal case where we don't have delay and the second is the real case. In Fig. 33 we have the ideal simulation of the divider.

 


Fig. 33 Simulation ideal frequency divider by 100

Here we can see how often we have a pulse in TC100, it repeats every 100 clock's when CE is '1' and we are not resetting.

Now we see the real case and we will have the delay between the input and output.

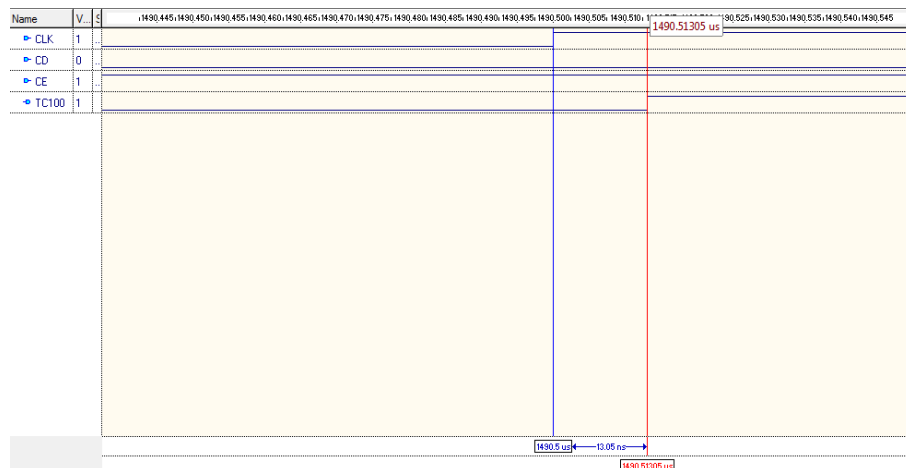


Fig. 34 Simulation real frequency divider by 100

In this Fig. 34 we can appreciate a delay between CLK and TC100 of 13,05 ns.

1.3.2.2.3 The frequency divider by 2

 


Fig. 35 Schematic of frequency divider by 2

The code of this block is very similar with the frequency divider by 50 and 100.

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY Freq_Div_2 IS
    PORT(CD,CLK,CE : IN std_logic;
          TC2 : OUT std_logic);
END Freq_Div_2;

ARCHITECTURE FSM_like OF Freq_Div_2 IS
    CONSTANT Max_Count : STD_LOGIC := '1';
    CONSTANT Reset : STD_LOGIC := '0';

    -- Internal state machine wires --
    SIGNAL present_state,future_state: STD_LOGIC := Reset;
    -- Remember that this idea of "=" Reset;" initialising the wires, has sense only for the simulator, not
    -- for a real synthesised flatened circuit, in which CD is used to reset the flip-flops

BEGIN
    ----- the only clocked block : the state register
    state_register: PROCESS (CD, CLK)
    BEGIN
        IF CD = '1' THEN -- reset counter
            present_state <= Reset;
        ELSIF (CLK'EVENT and CLK = '1') THEN -- Synchronous register (D-type flip-flop)
            present_state <= future_state;
        END IF;
    END PROCESS state_register;

    ----- CC1: combinational circuit for calculating next state
    CC1: PROCESS (present_state, CE)
    BEGIN
        IF CE = '1' THEN
            IF (present_state = Reset ) THEN
                future_state <= Max_Count; --(only 2 states, no need to add )
            ELSE
                future_state <= Reset;
            END IF;
        ELSE
            future_state <= present_state; -- count disable
        END IF;
    END PROCESS CC1;

    ----- CC2: combinational circuit for calculating extra outputs
    TC2 <= '1' WHEN ((present_state = Max_count)AND CE = '1') ELSE '0'; --terminal count
END FSM_like;

```

Fig. 36 Schematic of multiplier

In the Fig. 37 we have the simulation.

 


Fig. 37 Simulation frequency divider by 2

In the simulation we check that every two clock’s we have a pulse in output. To finish we are doing a T-Flip-Flop.

1.3.2.2.4 The T_Flip_Flop

Finally we are doing a T-Flip-Flop that we can see in Fig. 38

 


Fig. 38 Schematic of T-Flip-Flop

The code of this block is in Fig. 39

```

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;
USE IEEE.STD_LOGIC_UNSIGNED.all;

ENTITY T_Flip_Flop IS
    Port (
        CLK      : IN  STD_LOGIC;
        CD       : IN  STD_LOGIC;
        T        : IN  STD_LOGIC;
        Q        : OUT STD_LOGIC
    );
END T_Flip_Flop;

-- Internal description in FSM style
ARCHITECTURE FSM_like OF T_Flip_Flop IS

    CONSTANT Reset : STD_LOGIC := '0';

    -- Internal wires
    SIGNAL present_state, future_state: STD_LOGIC := Reset;
    -- This thing of initialising these signals to the "Reset" state,
    -- is only an issue for the functional simulator. Once the circuit
    -- is synthesised, this thing is completely irrelevant.

    BEGIN
        ----- the only clocked block : the state register
        state_register: PROCESS (CD, CLK)
            BEGIN
                IF CD = '1' THEN
                    present_state <= Reset;
                ELSIF (CLK'EVENT and CLK = '1') THEN
                    present_state <= future_state;
                END IF;
            END PROCESS state_register;

            ----- next state logic
            -- A T flip flop invert the output when T = 1, and do nothing when T = 0
            CS_1: PROCESS (present_state, T)
                BEGIN
                    IF T = '1' THEN
                        future_state <= NOT (present_state);
                    ELSE
                        future_state <= present_state;
                    END IF;
                END PROCESS CS_1;

            ----- CS_2: combinational system for calculating extra outputs
            -- Very simple in this case, a buffer.
            Q <= present_state;

        END FSM_like;
    
```

Fig. 39 Code in VHDL of T-Flip-Flop

We see the simulation in the Fig. 40 and we check the proper operation.

 


Fig. 40 Simulation T-FF

1.3.2.3 The Timer

Now we are study the timer that we see in Fig. 41.

 


Fig. 41 Schematic of Timer

In Fig. 42 we have the code of this timer and we can see that this block has two blocks inside: the control timer and a counter.

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY timer IS
    PORT(
        CD          : IN std_logic;
        TRIG        : IN std_logic;
        CLK         : IN std_logic;
        TIME_BASE   : IN std_logic;
        TIMER_OUT   : OUT std_logic
    );
END timer;

ARCHITECTURE schematic OF timer IS
    -- Components
    COMPONENT control_unit_timer IS
        PORT(
            TRIG,TC5,CD,CLK : IN std_logic;
            Enable,Clear    : OUT std_logic
        );
    END COMPONENT;

    COMPONENT counter IS
        PORT(
            CD,CLK,CE : IN std_logic;
            Q         : OUT std_logic_vector (2 downto 0);
            TC8      : OUT std_logic
        );
    END COMPONENT;

    -- Signals for connecting components together (just the internal wires)
    SIGNAL CE, Clear, TC5, Q0, Q1, Q2, Z, TC8 : std_logic;

    BEGIN
    -- Instantiation of components

```

```

FSM : control_unit_timer
PORT MAP (
    -- from component name => to signal or port name
    TRIG => TRIG,
    CLK  => CLK,
    CD   => CD,
    Clear=> Clear,
    Enable=> CE,
    TCS  => TC5
);

three_bit_Counter : counter
PORT MAP (
    CLK => TIME_BASE,
    CD  => Clear,
    CE  => CE,
    TC8 => TC8,
    Q(0) => Q0,
    Q(1) => Q1,
    Q(2) => Q2
);

--Detector '5'
Z <= NOT(Q1);
TC5 <= (Q0 AND Z AND Q2);
-- The output ports that have to be connected to signals
TIMER_OUT <= CE;
END schematic ;

```

Fig. 42 Code in VHDL of Timer

Inside this timer we have two blocks: a counter and a control unit timer that we can see in Fig. 43.

 


Fig. 43 Schematic inside of Timer

1.3.2.3.1 The Counter

We will perform a counter to eight as show in Fig. 44.

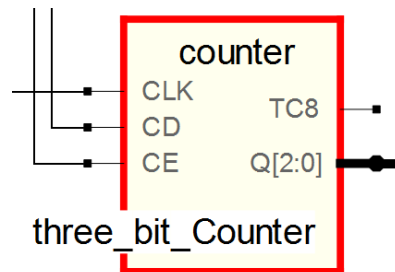


Fig. 44 Schematic of counter

In the code of Fig. 45 we can see that the counter goes from 0 to 7 depending the value of CE.

```

LIBRARY ieee;
USE IEEE.Std_Logic_1164.all;
USE IEEE.Std_Logic_Arith.all;
USE IEEE.Std_Logic_Unsigned.all;

ENTITY counter IS
  Port (
    CLK : IN Std_Logic;
    CD   : IN Std_Logic;
    CE   : IN Std_Logic;
    Q    : OUT Std_Logic_Vector(2 DOWNTO 0);
    TC8  : OUT Std_Logic
  );
END counter;

-- Internal description in FSM style
ARCHITECTURE FSM_like OF counter IS
  -- Internal wires
  -- State signals declaration
  TYPE State_type IS (Num0, Num1, Num2, Num3, Num4, Num5, Num6, Num7);
  -----> This is important: specifying to the synthesiser the code for the states
  ATTRIBUTE syn_enum_encoding : STRING;
  ATTRIBUTE syn_enum_encoding OF State_type : TYPE IS "sequential";
  -- (It may be: "sequential" (binary); "gray"; "one-hot", etc.
  SIGNAL present_state, future_state : State_type;

  -- Constants for special states (the first and the last state)
  CONSTANT Reset : State_type := Num0; -- The first state. This is another name for the state Num0
  CONSTANT Max_count : State_type := Num7; -- The last state. This is another way to name the state Num7

BEGIN
  ----- State Register: the only clocked block.
  state_register: PROCESS (CD, CLK)
  BEGIN
    IF CD = '1' THEN -- reset counter
      present_state <= Reset;
    ELSIF (CLK'EVENT and CLK = '1') THEN -- Synchronous register (D-type flip-flop)
      present_state <= future_state;
    END IF;
  END PROCESS state_register;

  ----- CC1: Combinational system for calculating next state
  CC_1: PROCESS (present_state, CE)
  BEGIN
    IF CE = '0' THEN
      future_state <= present_state; -- count disable
    ELSE -- just a simple state up count
      CASE present_state IS
        WHEN Num0 =>
          future_state <= Num1;
        WHEN Num1 =>
          future_state <= Num2;
        WHEN Num2 =>
          future_state <= Num3;
        WHEN Num3 =>
          future_state <= Num4;
        WHEN Num4 =>
          future_state <= Num5;
        WHEN Num5 =>
          future_state <= Num6;
        WHEN Num6 =>
          future_state <= Num7;
        WHEN Num7 =>
          future_state <= Num0;
      END CASE;
    END IF;
  END PROCESS CC_1;

  CC_2: PROCESS (present_state, CE)
  BEGIN
    -- The terminal count output
    IF ((present_state = Max_count) AND (CE = '1')) THEN
      TC8 <= '1';
    ELSE
      TC8 <= '0';
    END IF;

    -- And now just copying the present state to the output:
    CASE present_state IS
      WHEN Num0 =>
        Q <= "000";
      WHEN Num1 =>
        Q <= "001";
      WHEN Num2 =>
        Q <= "010";
      WHEN Num3 =>
        Q <= "011";
      WHEN Num4 =>
        Q <= "100";
      WHEN Num5 =>
        Q <= "101";
      WHEN Num6 =>
        Q <= "110";
      WHEN Num7 =>
        Q <= "111";
    END CASE;
  END PROCESS CC_2;
END FSM_like;

```

Fig. 45 Code in VHDL of counter

1.3.2.3.2 The Control Unit Timer

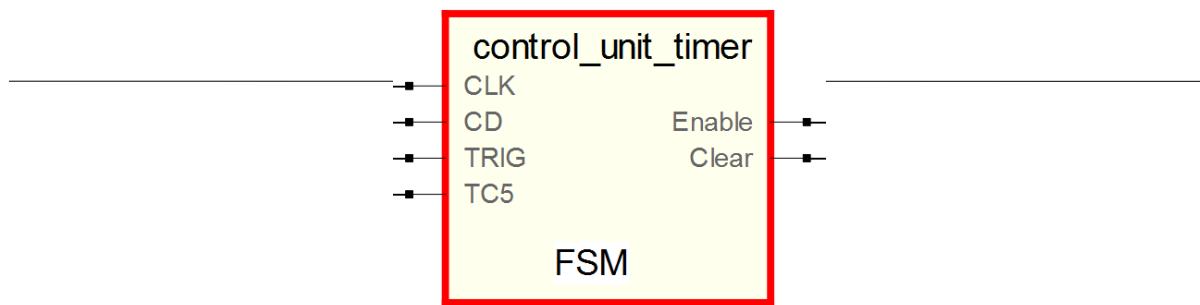


Fig. 46 Schematic of control unit timer

In Fig. 46 we have the control unit timer. In the code of the control unit timer (Fig. 47) we can see that depending the inputs (if we are in case idle, clear_s or count) we will have different values in outputs enable and clear.

```

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;
USE IEEE.STD_LOGIC_ARITH.all;
USE IEEE.STD_LOGIC_UNSIGNED.all;

ENTITY control_unit_timer IS
    Port (
        CLK      : IN  STD_LOGIC;
        CD       : IN  STD_LOGIC;
        TRIG     : IN  STD_LOGIC;
        TCS      : IN  STD_LOGIC;
        Enable   : OUT STD_LOGIC;
        Clear    : OUT STD_LOGIC
    );
END control_unit_timer;

-- Internal description in FSM style
ARCHITECTURE FSM_like OF control_unit_timer IS
    -- Internal wires
    TYPE State_type IS (Idle, Clear_s, Count);
    -----> This is important: specifying to the synthesiser the code for the states
    ATTRIBUTE syn_enum_encoding : STRING;
    ATTRIBUTE syn_enum_encoding OF State_type : TYPE IS "sequential";
    -- (It may be: "sequential" (binary); "gray"; "one-hot", etc.
    SIGNAL present_state, future_state : State_type ;

    -- Constants for special states (the first and the last state)
    CONSTANT Reset : State_type := Idle; -- The first state. This is another name for the state Idle
    CONSTANT Max_count : State_type := Count; -- The last state. This is another way to name the state Count

    BEGIN
    ----- State Register: the only clocked block.
    ----- The "memory" of the system (future events will depend on past events)
    state_register: PROCESS (CD,CLK)
        BEGIN
        IF CD='1' THEN -- reset counter
            present_state <= Reset;
        ELSIF (CLK'EVENT and CLK = '1') THEN -- Synchronous register (D-type flip-flop)
            present_state <= future_state;
        END IF;
    END PROCESS state_register;

    ----- CC1: Combinational system for calculating next state
    CC_1: PROCESS (present_state, TRIG, TC5)
        BEGIN
        CASE present_state IS
            WHEN Idle =>
                IF TRIG = '0' THEN
                    future_state <= present_state;
                ELSIF (TRIG = '1') THEN
                    future_state <= Clear_s ;
                END IF;
            WHEN Clear_s =>
                future_state <= Count ;
            WHEN Count =>
                IF TC5='0' THEN
                    future_state <= present_state;
                ELSE
                    future_state <= Idle ;
                END IF;
        END CASE;
    END PROCESS CC_1;

    CC_2: PROCESS (present_state)
        BEGIN
        -- The terminal count output
        -- And now just copying the present state to the output:
        CASE present_state IS
            WHEN Idle =>
                Enable <= '0';
                Clear <= '0';
            WHEN Clear_s =>
                Enable <= '0';
                Clear <= '1';
            WHEN Count =>
                Enable <= '1';
                Clear <= '0';
        END CASE ;
    END PROCESS CC_2;
    END FSM_like;

```

Fig. 47 Code in VHDL of Control Unit Timer

1.3.2.4 The Binary to BCD converter of 8 bit

This block has for input a binary number of 8 bits and the outputs are this number converted to BCD in units, tens and hundreds. For do this we need another block, it is the binary to BCD type 74185.

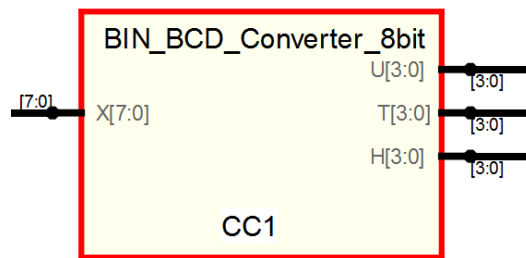


Fig. 48 Schematic of Binary to BCD converter

The code of the binary to BCD converter of 8 bit is in this Fig. 49

```

-----
-- A sample design for building circuits cascading
-- basic blocks
-----
-- A BIN_BCD_Converter_8bit
-----

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY BIN_BCD_Converter_8bit IS
    PORT (
        X      : IN  STD_LOGIC_VECTOR (7 DOWNTO 0);
        U      : OUT STD_LOGIC_VECTOR (3 DOWNTO 0);
        T      : OUT STD_LOGIC_VECTOR (3 DOWNTO 0);
        H      : OUT STD_LOGIC_VECTOR (3 DOWNTO 0);
    );
END BIN_BCD_Converter_8bit;

ARCHITECTURE estructura_en_cascada OF BIN_BCD_Converter_8bit IS

    -- The elemental component to be used:
    COMPONENT Bin_BCD_type74185 IS
        port (
            A,B,C,D,E      : in STD_LOGIC;
            Y              : out STD_LOGIC_VECTOR(6 DOWNTO 1)
        );
    END COMPONENT;

    -- Signals
    SIGNAL K              : STD_LOGIC_VECTOR (8 DOWNTO 0);

BEGIN
    -- Instantiation of up to 3 basic 1-BIN-BCD:
    adder_0 : Bin_BCD_type74185
        PORT MAP (
            A      -- from component name => to signal or port name
            => X(3),
            B      => X(4),
            C      => X(5),
            D      => X(6),
            E      => X(7),
            Y(1)  => K(0),
            Y(2)  => K(1),
            Y(3)  => K(2),
            Y(4)  => K(3),
            Y(5)  => K(4),
            Y(6)  => K(5)
        );
    adder_1 : Bin_BCD_type74185
        PORT MAP (
            A      -- from component name => to signal or port name
            => X(1),
            B      => X(2),
            C      => K(0),
            D      => K(1),
            E      => K(2),
            Y(1)  => U(1),
            Y(2)  => U(2),
            Y(3)  => U(3),
            Y(4)  => T(0),
            Y(5)  => K(6),
            Y(6)  => K(7)
        );
    adder_2 : Bin_BCD_type74185
        PORT MAP (
            A      -- from component name => to signal or port name
            => K(6),
            B      => K(3),
            C      => K(4),
            D      => K(5),
            E      => '0',
            Y(1)  => T(1),
            Y(2)  => T(2),
            Y(3)  => T(3),
            Y(4)  => H(0),
            Y(5)  => H(1),
            Y(6)  => K(8)
        );

    U(0) <= X(0);
    H(2) <= '0';
    H(3) <= '0';
END estructura_en_cascada;

```

Fig. 49 Code in VHDL of binary to BCD converter

The circuit inside the binary to BCD converter is in Fig. 50. In this figure we can see the next block: the binary to BCD type 74185.

 


Fig. 50 Schematic inside the binary to BCD converter

1.3.2.4.1 The Binary to BCD type 74185

The code of this block is in Fig. 51. We can see the true table of this converter, the input of each block has 5 bits and in the outputs we have 6 bits.

```

library ieee;
use ieee_std_logic_1164.all;

entity Bin_BCD_type74185 is
    port (
        A,B,C,D,E      : in STD_LOGIC;
        V               : out STD_LOGIC_VECTOR(6 DOWNTO 1)
    );
end Bin_BCD_type74185;

-- EL vector d'entrada és: V_ENT(4) = E; V_ENT(3) = D; V_ENT(2) = C; V_ENT(1) = B; V_ENT(0)=A
-- EL vector de sortida és V_SOR(5) = Y(1); V_SOR(4) = Y(2); V_SOR(3) = Y(3); V_SOR(2) = Y(4); V_SOR(1) = Y(5); V_SOR(0) = Y(6)

architecture Arch_Taula_Veritat of Bin_BCD_type74185 is

    SIGNAL V_ENT      : STD_LOGIC_VECTOR (4 DOWNTO 0);
    SIGNAL V_SOR      : STD_LOGIC_VECTOR (5 DOWNTO 0);

begin

    with V_ENT select
    ---
    ---
    V_SOR <= "000000" when "00000",
             "000001" when "00001",
             "000010" when "00010",
             "000011" when "00011",
             "000100" when "00100",
             "001000" when "00101",
             "001001" when "00110",
             "001010" when "00111",
             "001011" when "01000",
             "001100" when "01001",
             "010000" when "01010",
             "010001" when "01011",
             "010010" when "01100",
             "010011" when "01101",
             "010100" when "01110",
             "011000" when "01111",
             "011001" when "10000",
             "011010" when "10001",
             "011011" when "10010",
             "011100" when "10011",
             "100000" when "10100",
             "100001" when "10101",
             "100010" when "10110",
             "100011" when "10111",
             "100100" when "11000",
             "101000" when "11001",
             "101001" when "11010",
             "101010" when "11011",
             "101011" when "11100",
             "101000" when "11101",
             "110000" when "11110",
             "110001" when "11111" when others;

    V_ENT(4) <= E;
    V_ENT(3) <= D;
    V_ENT(2) <= C;
    V_ENT(1) <= B;
    V_ENT(0) <= A;

    Y(6) <= V_SOR(5);
    Y(5) <= V_SOR(4);
    Y(4) <= V_SOR(3);
    Y(3) <= V_SOR(2);
    Y(2) <= V_SOR(1);
    Y(1) <= V_SOR(0);

end Arch_Taula_Veritat;

```

Fig. 51 Code in VHDL of binary to BCD type 74185

1.3.2.5 The Quad_Mux4

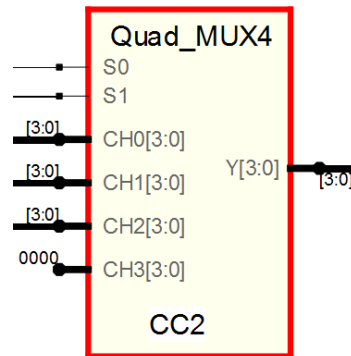


Fig. 52 Schematic of Quad Mux4

The code of the Quad_Mux4 is in Fig. 53 and we can see a multiplexor that depending the values of S1 and S0, we have I output CH0, CH1, CH2 or CH3.

```

library ieee;
use ieee.std_logic_1164.all;

entity Quad_MUX4 is
PORT(
    CH0      :IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    CH1      :IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    CH2      :IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    CH3      :IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    Y        :OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    S0,S1    :IN STD_LOGIC
);

end Quad_MUX4;

architecture archMUX of Quad_MUX4 is
begin
    Y <= CH0 WHEN S0='0' AND S1='0' ELSE
        CH1 WHEN S0='1' AND S1='0' ELSE
        CH2 WHEN S0='0' AND S1='1' ELSE
        CH3 WHEN S0='1' AND S1='1';
end archMUX;

```

Fig. 53 Code in VHDL of Quad Mux4

1.3.2.6 The BCD to 7 segments

Finally, to see the result we are going to convert of BCD to 7 segments.

 


Fig. 54 Schematic of BCD to 7seg

The code of the BCD to 7 segments is in Fig. 55.

```

-- A sample design in which has to be programmed the functionality of: RBI_L, RBO_L i IT_L
-- Make a project for this file.
-- Add the functionality of the IT_L signal and synthesise again
-- Add the functionality of the RBI_L signal and synthesise again
-- Finally, add the output RBO_L and synthesise again

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;

ENTITY BCD_7seg IS
    PORT (
        X      : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        H_SYM  : IN STD_LOGIC;
        Y      : OUT STD_LOGIC_VECTOR (6 DOWNTO 0)
    );
END BCD_7seg;

-- EL vector d'entrada és: V_ENT(3) = D; V_ENT(2) = C; V_ENT(1) = B; V_ENT(0) = A;
-- EL vector de sortida és V_SOR(6) = a; V_SOR(5) = b; V_SOR(4) = c; V_SOR(3) = d;
-- V_SOR(2) = e; V_SOR(2) = f; V_SOR(0) = g;

-- Descripció de l'arquitectura del bloc a partir de la TdV

ARCHITECTURE Arch_Taula_Veritat OF BCD_7seg IS
BEGIN
    PROCESS (H_SYM, X)
    BEGIN
        IF H_SYM = '0' THEN
            CASE X IS
                -- DCBA          abcdefg
                -- El NOT representa sortides actives a nivell baix
                WHEN "0000" => Y <= ("1111110"); -- 0
                WHEN "0001" => Y <= ("0110000"); -- 1
                WHEN "0010" => Y <= ("0110000"); -- 2
                WHEN "0011" => Y <= ("1101101"); -- 3
                WHEN "0100" => Y <= ("1111001"); -- 4
                WHEN "0101" => Y <= ("0110011"); -- 5
                WHEN "0110" => Y <= ("1011011"); -- 6
                WHEN "0111" => Y <= ("1011111"); -- 7
                WHEN "1000" => Y <= ("1110000"); -- 8
                WHEN "1001" => Y <= ("1111111"); -- 9
                WHEN "1010" => Y <= ("1110011"); -- A
                WHEN "1011" => Y <= ("1110111"); -- B
                WHEN "1100" => Y <= ("0011111"); -- C
                WHEN "1101" => Y <= ("1001110"); -- D
                WHEN "1110" => Y <= ("0111101"); -- E
                WHEN "1111" => Y <= ("1001111"); -- F
                WHEN others => Y <= ("1000111"); -- F
            END CASE;
        ELSE Y <= ("0110111");
        END IF;
    END PROCESS;
END Arch_Taula_Veritat;

```

Fig. 55 Schematic of multiplier

1.3.3 Total design

For show the result of this design, we can see in these figures the real result. In Fig. 56 we can see that we introduce a 3 and a 7 (the buttons we can see at the bottom); in Fig. 57 we pulse start and we can see the units and the tens of the result (and a led lights); and finally in Fig. 58 we pulse the other button for show the hundreds while the led is lit.

 


Fig. 56 Multiplier



Fig. 57 Multiplier



Fig. 58 Multiplier