

BACHELOR DEGREE IN TELECOMMUNICATIONS, Digital Circuits and Systems (CSD), March 21, 2017. Grades will be available on March 25. Questions about the exam: [Instructors' office time](#). It is mandatory to explain all the steps that you follow to solve each exercise in order to get grades. A student interview about the submitted work can also be requested.

Individual Test 1

The entity represented in Fig. 1a is an electronic dice decoder, a combinational block for adapting the binary numbers from 1 to 6 to a 7-LED display that has the typical layout shown in Fig. 1b. Codes "000" and "111" don't care.

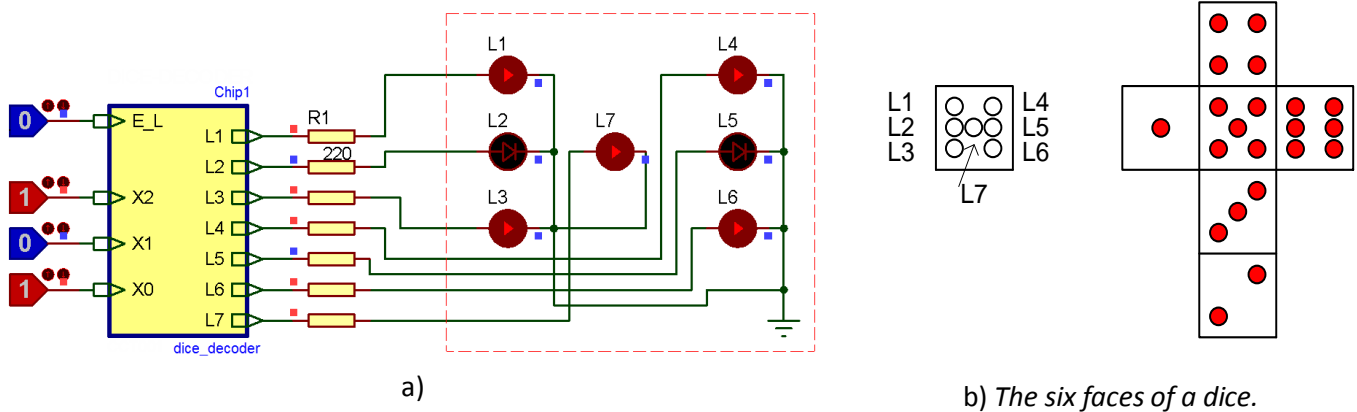


Fig. 1 Circuit for driving an electronic dice decoder. A version of this circuit runs [here](#) in Proteus.

1. Deduce the decoder truth table of all the outputs $L_i = f(E_L, X2, X1, X0)$.
2. Describe the algebraic expression of **L3** as a product of maxterms.
3. Describe the algebraic expression of **L1** as a sum of minterms.
4. Express the output **L6** using only NAND.
5. Implement the output **L7** using the method of multiplexers and a MUX4 component.
6. Draw a behavioural flow chart and translate it to a VHDL file for the *dice_decoder*.
7. Using the method of decoders and a *Decoder_3_8* component, draw a schematic for the *dice_decoder* and write it in VHDL file. How many files are required?
8. If the following table in Fig. 2 represents the output from Minilog when inputting the *dice_decoder* [truth table](#) and simplifying by **PoS**, write down the equations for the outputs **L4** and **L6**.

E	XXX	LLLLLLL
L210	1234567	
==	==	==
-11-		..11...
---1	1
--1-		.1..1..
-1--		11..11.
0---		1111111

Fig. 2 Output table format from Minilog.exe.

- a) Addition: (+116) + (-33)
- b) Subtraction: (-33) - (+100)
- c) Subtraction: (-100) - (-33)
- d) Addition: (-125) + (+125)

Fig. 3 Add and subtract in 8-bit 2C convention.

9. Solve the arithmetic operations in Fig. 3 using 8-bit 2C (two's complement) number representation. Indicate when there is an overflow situation (OV flag). Which is the valid range of the operands and operations?
10. Propose a circuit structure able to perform the 8-bit 2C operations in 9).