

Exam 1.

November 11th, 2020

Problem 1.

(0.5p each question)

The Fig. 1 shows the internal structure (technology view) of a standard classic HCT chip with the given electrical characteristics.


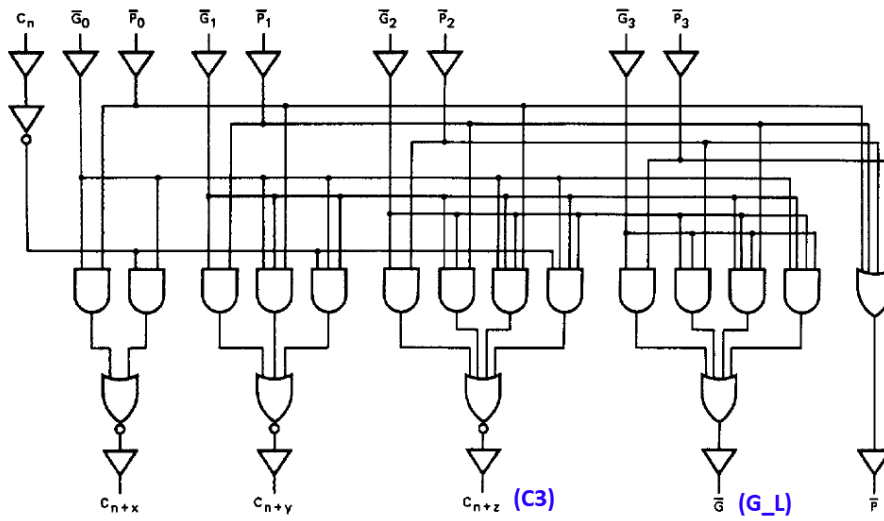


Fig. 1
Symbol, structure and electrical characteristics.

 

Characteristic	Symbol	V _{DD}	Max	Unit
Propagation Delay Time (one gate)	t _{PLH} , t _{PHL}	5.0 V	2.7	ns

V _{DD}	5.0 V	25°C	Symbol	Min	Typ #	Max
Output Voltage	"0" Level	V _{OL}	—	0.15 V	0.26 V	
	"1" Level	V _{OH}	3.98 V	4.32 V	—	
Input Voltage	"0" Level	V _{IL}	—	1.35 V	2.1 V	
	"1" Level	V _{IH}	2.4 V	3.15 V	—	

- Represent logic values, voltages and noise margins for this logic family.
- Calculate the chip's power consumption if each gate drains 0.56 μA and is powered at 5.0 V.
- Calculate limiting resistors for a pair of LED (V_{AK} = 1.8 V, I_{LED} = 4 mA) connected at output **G_L** active-low, output **C3** active-high.
- Which is the longest propagation path? Calculate the maximum speed of operation.
- Which VHDL simulation allows us to measure propagation time delays in a given signal transition? What is the minimum time that it takes to simulate the entire input stimulus?

Problem 2.

(0.5p each question)

The equation in Fig. 2 represents a truth table which is going to be solved in VHDL using the plan B (behavioural) and the plan C2 (hierarchical based on components).

$$T = f(D_1, D_0, A, B) = \prod M(1, 3, 6, 8, 10, 14)$$

Fig. 2
Truth table of a 4-input combinational circuit named *Circuit_T*

- Solve the function using a plan B, a behavioural approach. Represent a schematic or flowchart and explain how to translate it into VHDL.
- Solve the function **T** using the method of decoders (MoD).
- Solve the function **T** using the method of multiplexers (MoM) and a MUX_8.
- Invent a MUX_16 using components of the same kind (MUX_8, MUX_4, MUX_2) and logic gates if necessary.
- Solve the function **T** using the method of multiplexers (MoM) and MUX_16. How many VHDL files will contain this project?

Problem 3.

- a) Obtain the logic expression of the function $R = g(A, B, C)$ of the circuit in Fig. 3. (0.5p)
- b) Simplify the function to obtain a PoS or SoP. (0.5p)
- c) Draw the circuit's truth table and invent another equivalent circuit based on only-NAND of two inputs. (0.5p)
- d) Deduce the output R in the timing diagram of the circuit in Fig. 3 when the input stimulus is applied. If Min_Pulse is $2.55 \mu s$, how long does it take to run all the simulation of the stimulus represented? (1p)


 


Fig. 3
Combinational circuit based on logic gates. $R = g(A, B, C)$ and proposed stimulus file.

 

Problem 4.

We have in mind inventing the circuit in Fig. 4 for performing arithmetic and logic operations.

 


Fig. 4
Symbol and operations performed by the arithmetic and logic unit (ALU_4bit)

OP	Function	
00	$A + B$	Arithmetic (4-bit signed integer in two's complement)
01	$A - B$	Arithmetic (4-bit signed integer in two's complement)
10	$A \cdot B$	Logic AND
11	$A \oplus B$	Logic XOR

- a) Deduce some examples of the circuit's truth table solving the four operations for the following data (12 stimulus). Express inputs and outputs in the right radix and indicate *don't care* ('x') results when necessary. (0.5p)

A = "0101" B = "1010"
 A = "1111" B = "1001"
 A = "1000" B = "1000"

OP	A	B	R	S	OV	Z

- b) Propose an internal architecture for this ALU_{4bit} circuit based on plan C2. Use as a component a 4-channel quadruple multiplexer (Quad_MUX_4) and other blocks and logic gates if necessary. Determine how many VHDL file contain your architecture. (1p)
- c) Design flag indicators S, OV and Z using logic gates. (0.5p)
- d) Invent the XOR block using only NOR. (0.5p)