
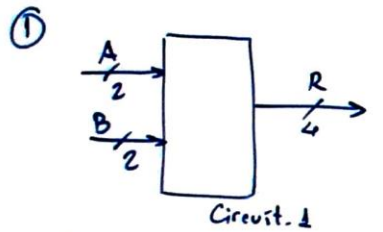


Problem 1

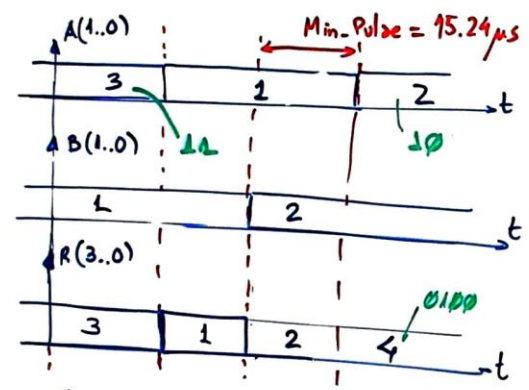


$R_i = f(B, B_0, A_i, A_0)$

To test all combinations  $\rightarrow 2^4$ . Min. Pulse = 243.84  $\mu$ s  
 The circuit is working as a 2-bit multiplier




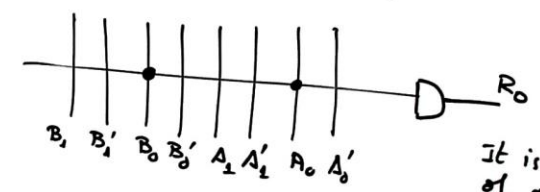③  $R_0 = m_5 + m_7 + m_{13} + m_{15}$   
 $= B_1' \cdot B_0 \cdot A_1' \cdot A_0 + B_1' \cdot B_0 \cdot A_1 \cdot A_0 + B_1 \cdot B_0 \cdot A_1' \cdot A_0 + B_1 \cdot B_0 \cdot A_1 \cdot A_0$   
 $= B_1' \cdot B_0 \cdot A_0 (A_1' + A_1) + B_1 \cdot B_0 \cdot A_0 (A_1' + A_1)$   
 $= B_1' \cdot B_0 \cdot A_0 + B_1 \cdot B_0 \cdot A_0 = B_0 \cdot A_0 (B_1' + B_1)$   
 $R_0 = B_0 \cdot A_0$




It is a simple product of only two literals

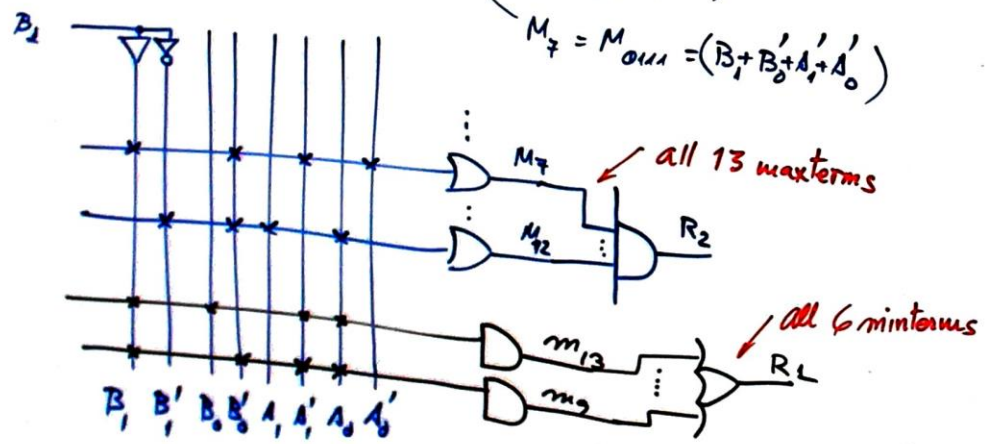②  $R_2 = \prod M(0, 1, 2, 3, 4, 5, 6, 7, 8, 9, 12, 13, 15)$   
 $M_{12} = M_{1100} = (B_1' + B_0' + A_1 + A_0)$   
 $M_7 = M_{0111} = (B_1 + B_0' + A_1' + A_0')$




$R_1 = \sum m(6, 7, 9, 11, 13, 14)$   
 $m_{13} = m_{1101} = B_1 \cdot B_0 \cdot A_1' \cdot A_0$   
 $m_9 = m_{1001} = B_1 \cdot B_0' \cdot A_1' \cdot A_0$

④  $R_3 = m_{15} = (B_1 \cdot B_0 \cdot A_1 \cdot A_0)'' = (B_1' + B_0' + A_1 + A_0)'$   
 NOR of 4 inputs  
 $((B_1' + B_0')') + ((A_1 + A_0)')'$   
 NOR-2

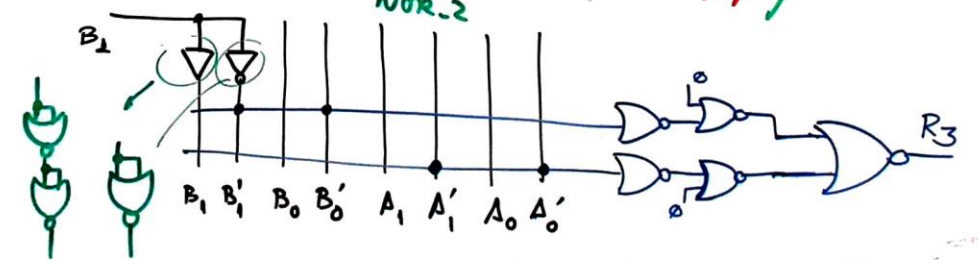

Problem 1

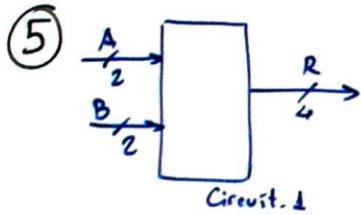

$$R_i = f(B, R_0, A_i, A_0)$$

- $R_3 \rightarrow 4$  levels of gates
- $R_2 \rightarrow 3$  levels
- $R_1 \rightarrow 3$  levels
- $R_0 \rightarrow 2$  levels


$$\Rightarrow t_p = 44 \text{ ns}$$

Circuit 1  
worst-case scenario


$$t_{p \text{ max}} = 11 \text{ ns}$$

one gate

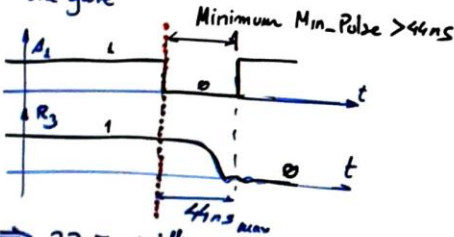Input switches  $\rightarrow$   
Output switches after  $t_p \rightarrow$



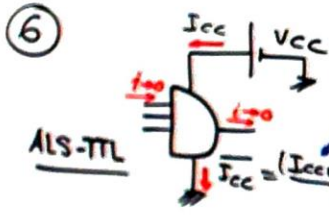$\Rightarrow 22.7$  Millions of operations per second



$$I_{cc} = \frac{(I_{ccu} + I_{ccd})}{2} = 2.65 \text{ mA}$$

static power consumption approximation


- $R_3 \rightarrow 5$  gates
- $R_2 \rightarrow 4$  gates
- $R_1 \rightarrow 7$  gates
- $R_0 \rightarrow 1$  gate

NOT, Buffer + 8 gates

$$35 \text{ gates} \Rightarrow P_s = V_{cc} \cdot I_{cc} (\text{Number of gates}) = 5V \cdot 2.65 \mu A \cdot 35$$

$$P_s = 463.75 \text{ mW}$$

⑦

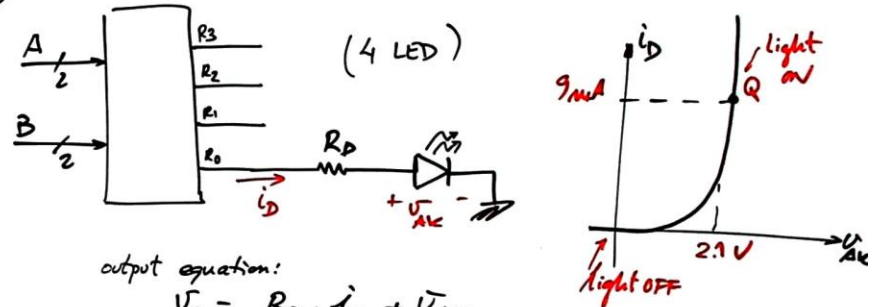


output equation:

$$V_o = R_D \cdot I_D + V_{AK}$$



when 'i'  $\rightarrow$  Light ON  $\rightarrow V_{o \text{ min}} = R_D I_{DQ} + V_{AKQ}$

$$R_D = \frac{V_{o \text{ min}} - V_{AKQ}}{I_{DQ}} = \frac{3V - 2.1V}{9 \mu A} = 100 \Omega$$

⑧ MoD

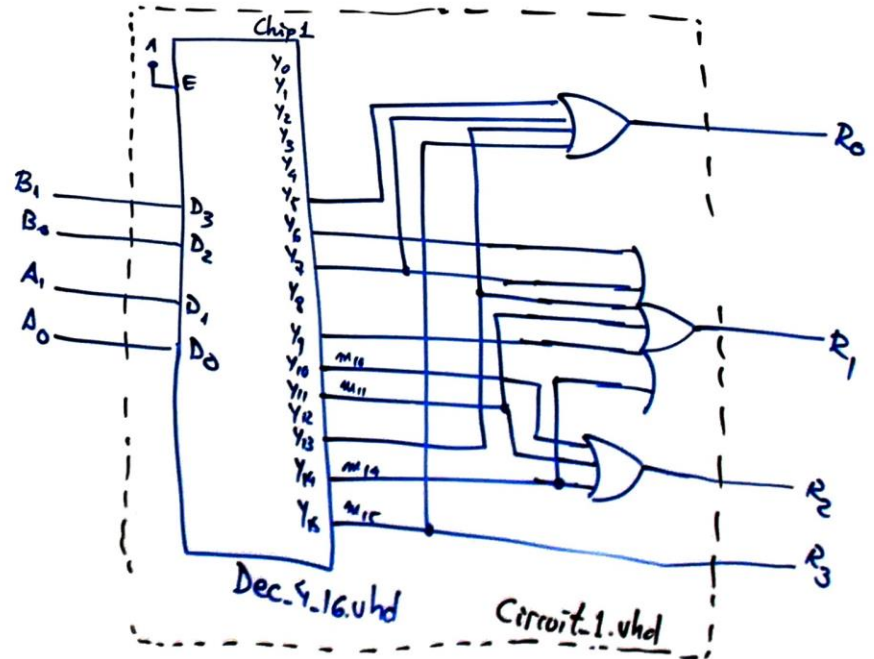

9) MoM using MUX2

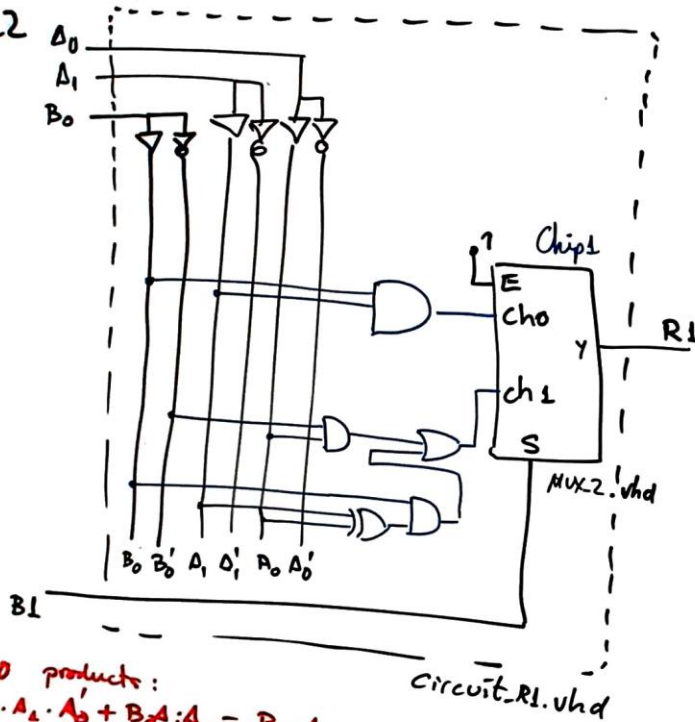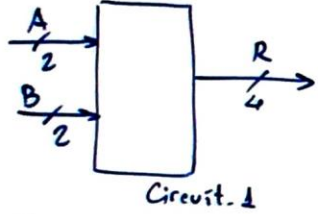


B <sub>1</sub>	B <sub>0</sub>	A <sub>1</sub>	A <sub>0</sub>	R <sub>1</sub>
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Ch0 products:  
 $B_0 \cdot A_1 \cdot A_0 + B_0 \cdot A_1 \cdot A_0 = B_0 \cdot A_1$

Ch1 products:  
 $B_0' \cdot A_1 \cdot A_0 + B_0' \cdot A_1 \cdot A_0 + B_0 \cdot A_1 \cdot A_0 + B_0 \cdot A_1 \cdot A_0'$   
 $B_0' \cdot A_1 \cdot A_0 + B_0 \cdot A_1 \cdot A_0$

10)  $R_0 = f(B_1, B_0, A_1, A_0)$

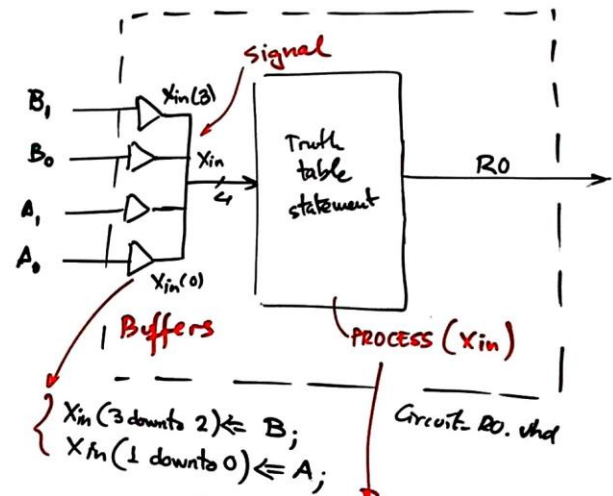

```

CASE X_in
  when "0000" => R0 <= '0';
  ...
  when "1110" => R0 <= '0';
  when others => R0 <= '1';
END CASE
    
```

Truth table