

Exam 2

May 31, 2019

Problem 1.

2.5p

The aim of the circuit in Fig. 1 is to activate a LED lamp during a time T , following the operating mode represented in Fig. 2.

- a) Draw a possible state diagram, indicating state transitions and outputs. Name states as S1, S2, etc.
- b) Draw and adapt the standard FSM architecture indicating signals and ports. How many D_FF (D-type flip flop) are required to implement this sequential circuit if the states are coded in binary sequential? Justify your response.
- c) Draw the CC1 truth table and its algorithmic state machine chart or flow chart.
- d) Draw the CC2 truth table and its algorithmic state machine chart or flow chart.

 


Fig. 1
Sequential circuit.

 


Fig. 2
Timing diagram that shows the circuit's mode of operation.

Problem 2.

2.5p

We want to implement a *Counter_mod14* (Fig. 3a) using a hierarchical strategy based on two components: a *Quad_MUX2* and a *Counter_mod16* (Fig. 3b).

- a) Draw an example timing diagram for the operating mode: $CE = '1'$ and $UD_L = '0'$.
- b) Plan the schematic of the *Counter_mod14* indicating the name of the signals and components involved. Explain how it works and the use of the multiplexer. How many *D_FF* the *Counter_mod14* will include?
- c) Explain and justify the truth table of the circuit to drive the *Quad_MUX2* selection input. Explain and justify the truth table for driving the *LD* input of the *Counter_mod16*.
- d) How many VHDL files are involved in this design? How the *Counter_mod16* component is organised internally: using the plan X (state enumeration) or using the plan Y (STD_LOGIC_VECTOR state signals)?

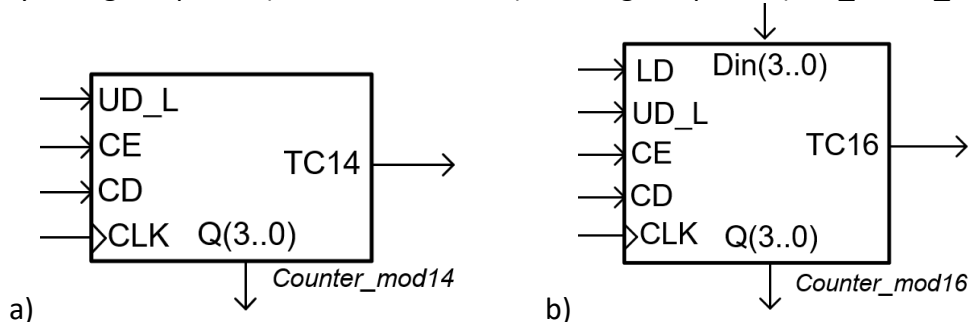


Fig. 3
Symbols for the top entity to be designed and one of the components.

Let's design a simple 2-wire asynchronous data transmitter based on a μC for sending to another computer a nibble (4-bits) of data. It is basically a right-shift register. The application symbol and pinning of the PIC18F4520 is represented in Fig. 4. We'll use the FSM style of programming in C language. The format for the serial output once the start-transmission ST rising edge is detected by means of an interrupt is: Start-bit ('0'), $Data_in(0)$, $Data_in(1)$, $Data_in(2)$, $Data_in(3)$; and then the end-of-transmission EoT pulse is generated to indicate that the transmitter has ended the process (see the Fig. 5). $Serial_out$ is held high when idle.

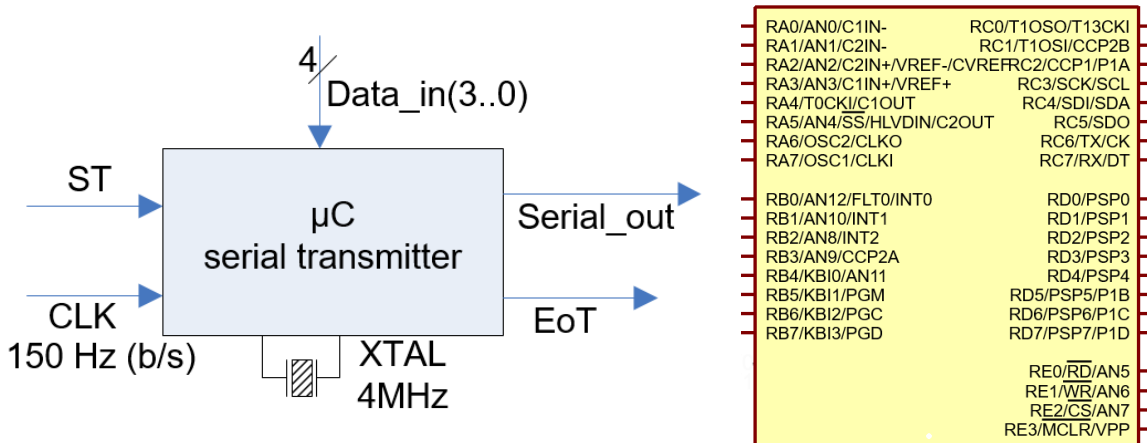


Fig. 4 Symbol of the data transmitter and the μC PIC18F4520 from Microchip.

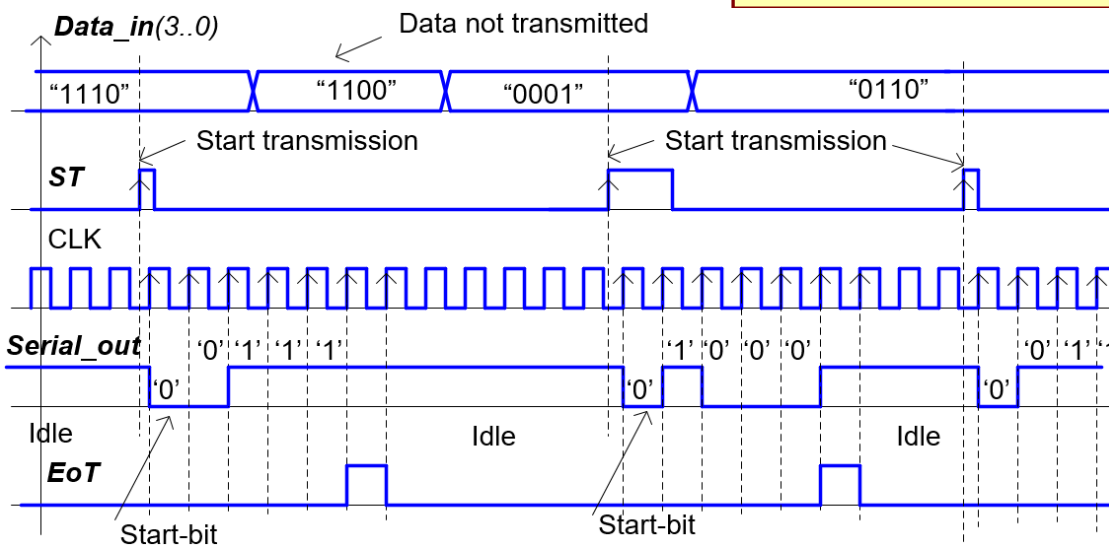


Fig. 5 Example of a section of a timing diagram where it can be seen how the data is read and right shifted in a single wire.

- Draw the hardware schematic. Reset circuit, XTAL oscillator, $Data_in(3..0) = (RA2, RA1, RD7, RD6)$, CLK (RB0), ST (RB1), $Serial_out$ (RC5), EoT (RC2). Explain how to configure the inputs and outputs in the $init_system()$.
- Draw the hardware/software diagram indicating the required RAM variables and how the FSM is solved in software. The transmission sequence will start when a rising edge is detected at the start ST push button by means of the interrupt INT1IF. The CLK input will generate an interrupt INTOIF so that a new bit is transmitted at a time at the $Serial_out$ as represented in Fig. 5. Transmission speed is 150 b/s.
- How $read_input()$ works to generate the $char$ variable var_Data_in ?
- How the variables var_Serial_out and var_EoT are written to the corresponding pins using $write_outputs()$ without interfering the other μC port pins?
- Which is the $ISR()$ used for? Propose the flow chart.
- Draw an state diagram showing the state transitions and the outputs for each state. Name the states, for instance: Idle, Start_bit, Data_0, Data_1, etc.
- Draw the truth tables and their equivalent flow charts for the $state_logic()$ and $output_logic()$.
- How to use and program the TMR0 peripheral in 8-bit mode to replace completely the functionality of the external CLK as the baud-rate generator?